

# Chapter 7

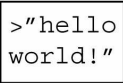

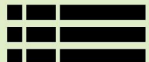
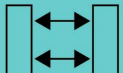
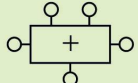

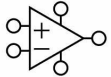
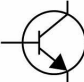

## ***Digital Design and Computer Architecture: ARM®*** **Edition**

Sarah L. Harris and David Money  
Harris



# Chapter 7 :: Topics


- Introduction
- Performance Analysis
- Single-Cycle Processor
- Multicycle Processor
- Pipelined Processor
- Advanced Microarchitecture

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	


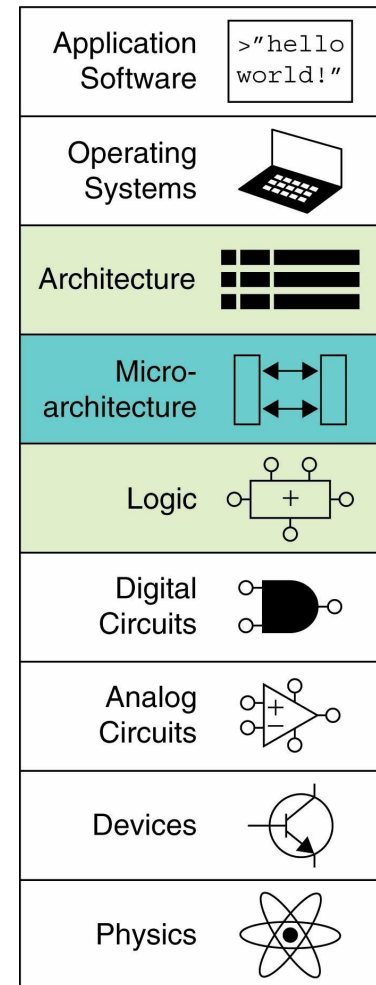
# Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- **Processor:**
  - **Datapath:** functional blocks
  - **Control:** control signals



# Microarchitecture

- Multiple implementations for a single architecture:
  - **Single-cycle:** Each instruction executes in a single cycle
  - **Multicycle:** Each instruction is broken up into series of shorter steps
  - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once



# Processor Performance

- **Program execution time**

**Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)**

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance



# ARM Processor

- Consider **subset** of ARM instructions:
  - **Data-processing instructions:**
    - **ADD, SUB, AND, ORR**
      - with register and immediate Src2, but **no shifts**
  - **Memory instructions:**
    - **LDR, STR**
      - with **positive immediate offset**
  - **Branch instructions:**
    - **B**




# Architectural State Elements

**Determines everything about a processor:**

- Architectural state:
  - 16 registers (including PC)
  - Status register
- Memory



# ARM Architectural State Elements

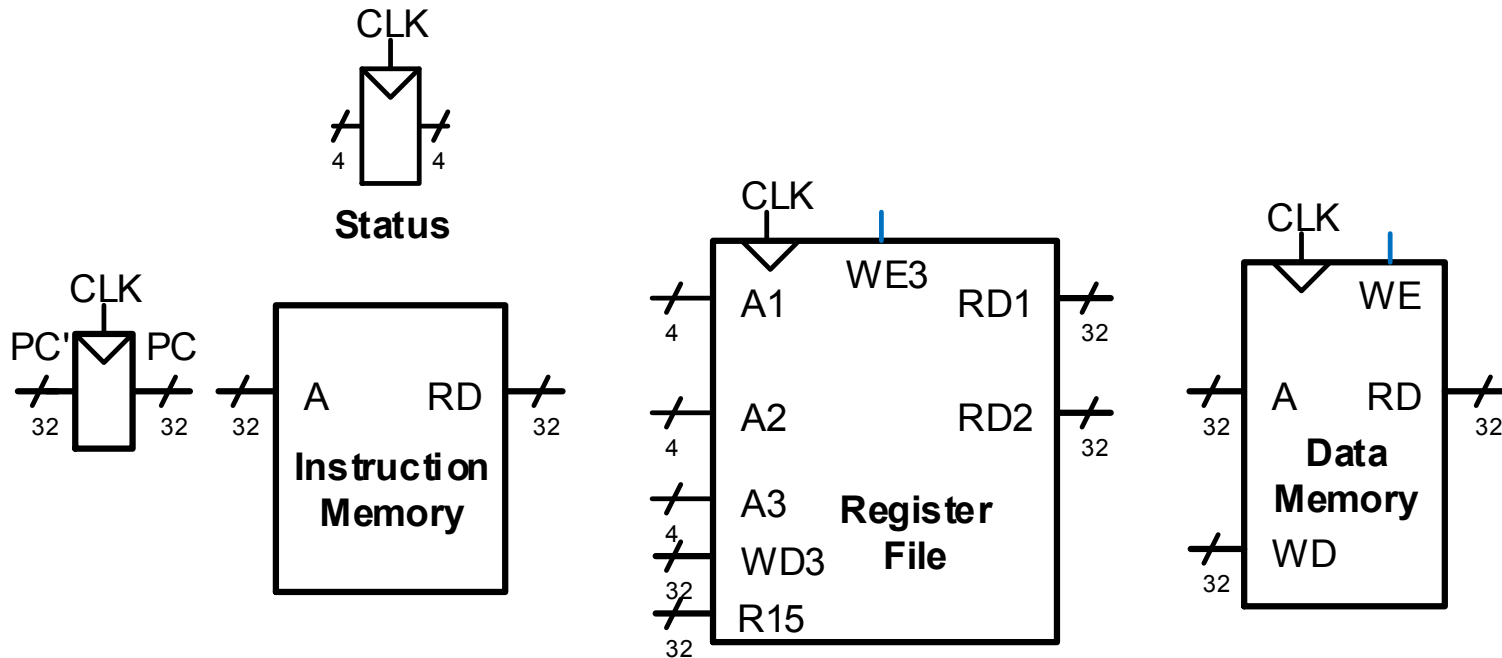



# Single-Cycle ARM Processor

- Datapath
- Control




# Single-Cycle ARM Processor

- **Datapath**
- Control



 
# Single-Cycle ARM Processor

- **Datapath:** start with LDR instruction
- **Example:** LDR R1, [R2, #5]  
LDR Rd, [Rn, imm12]





# Single-Cycle Datapath: LDR fetch

## STEP 1: Fetch instruction

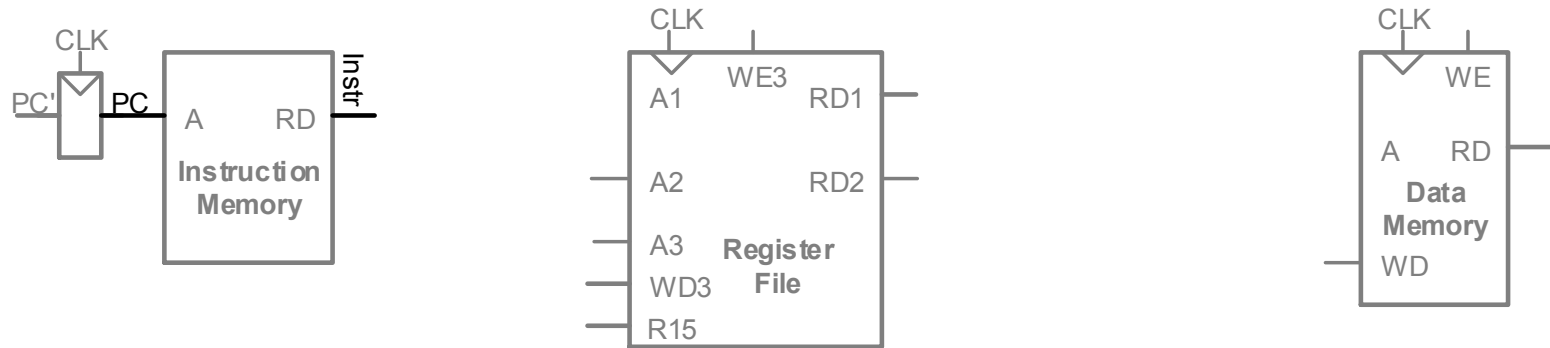



# Single-Cycle Datapath: LDR Reg Read

## STEP 2: Read source operands from RF

 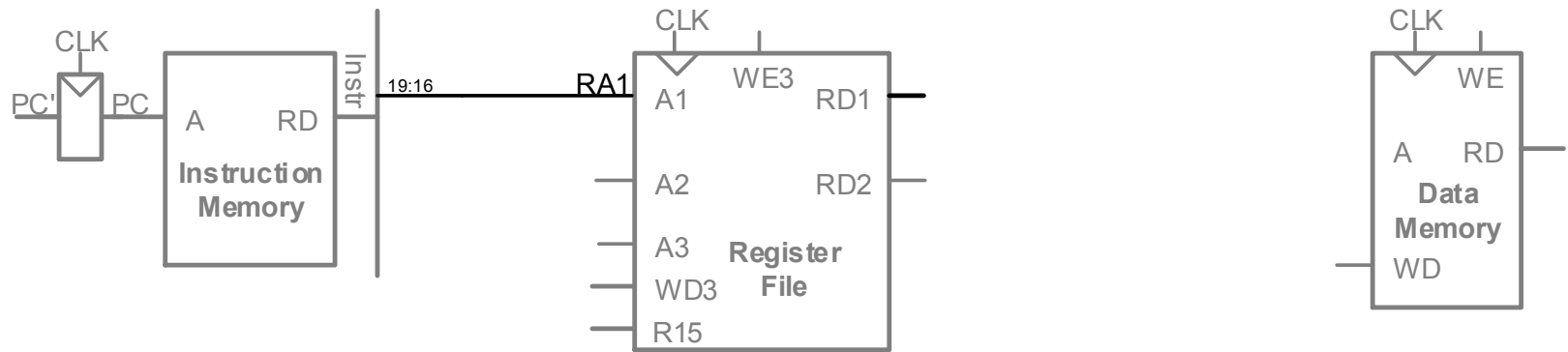



# Single-Cycle Datapath: LDR Immed.

## STEP 3: Extend the immediate

 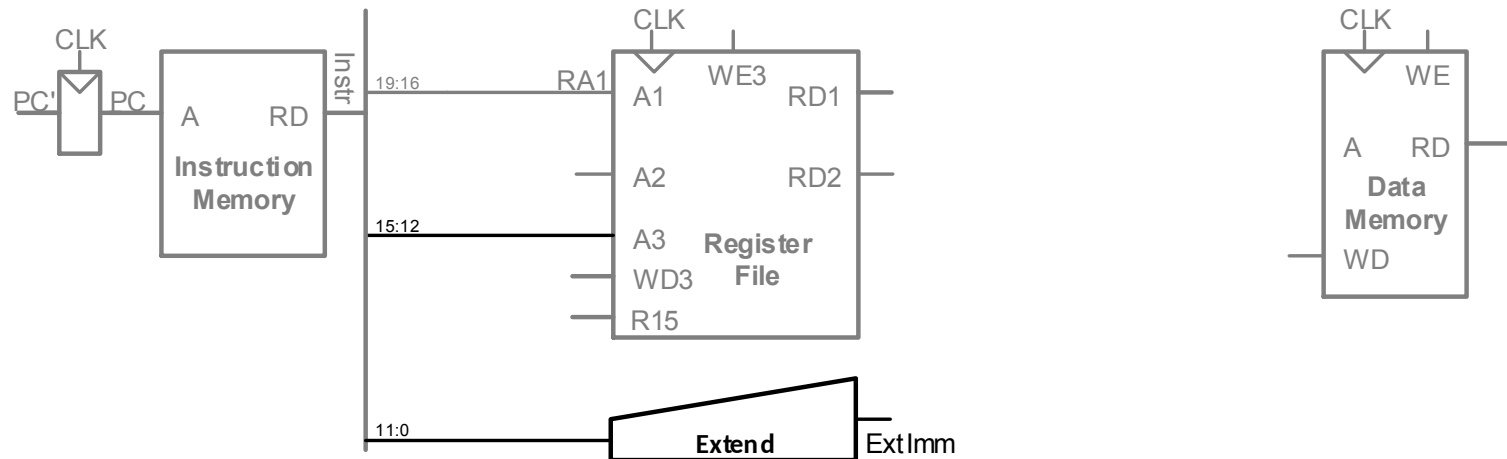



# Single-Cycle Datapath: LDR Address

## STEP 4: Compute the memory address

 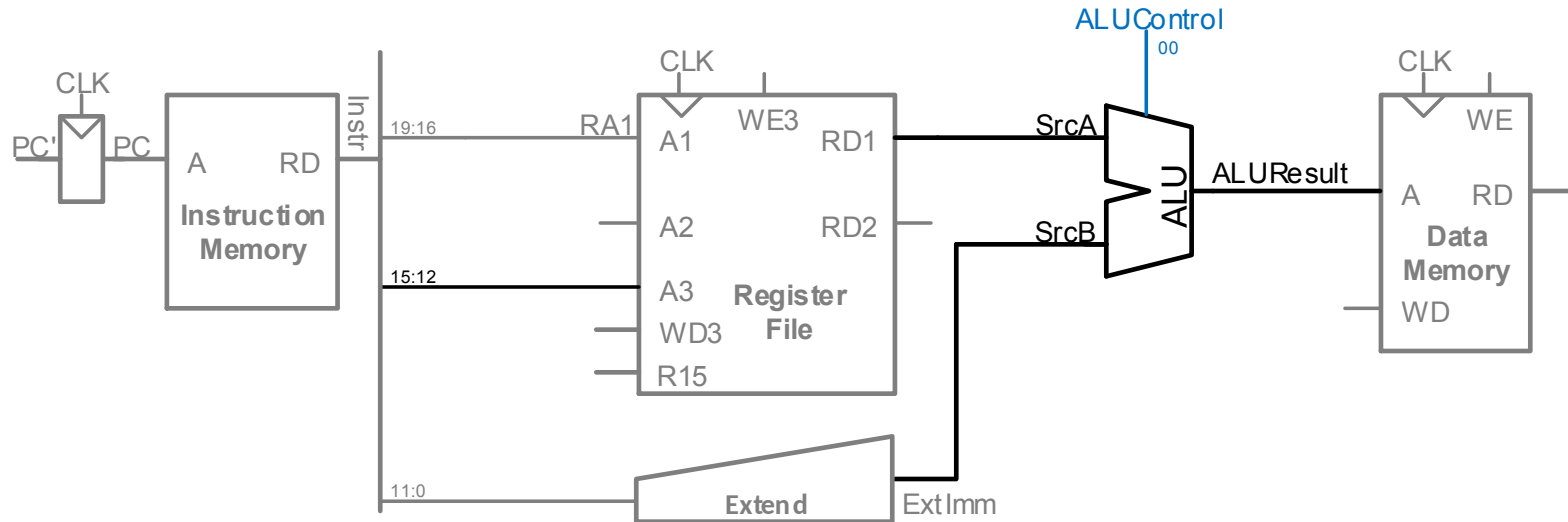
 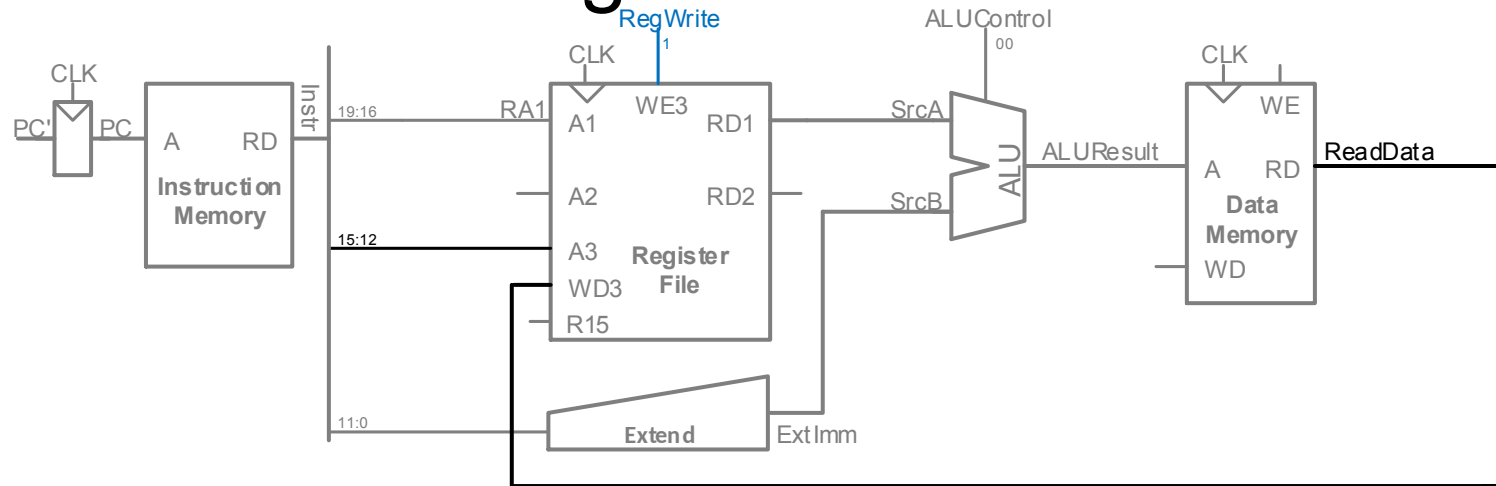
# Single-Cycle Datapath: LDR Mem Read


**STEP 5:** Read data from memory and write it back to register file






# Single-Cycle Datapath: PC Increment
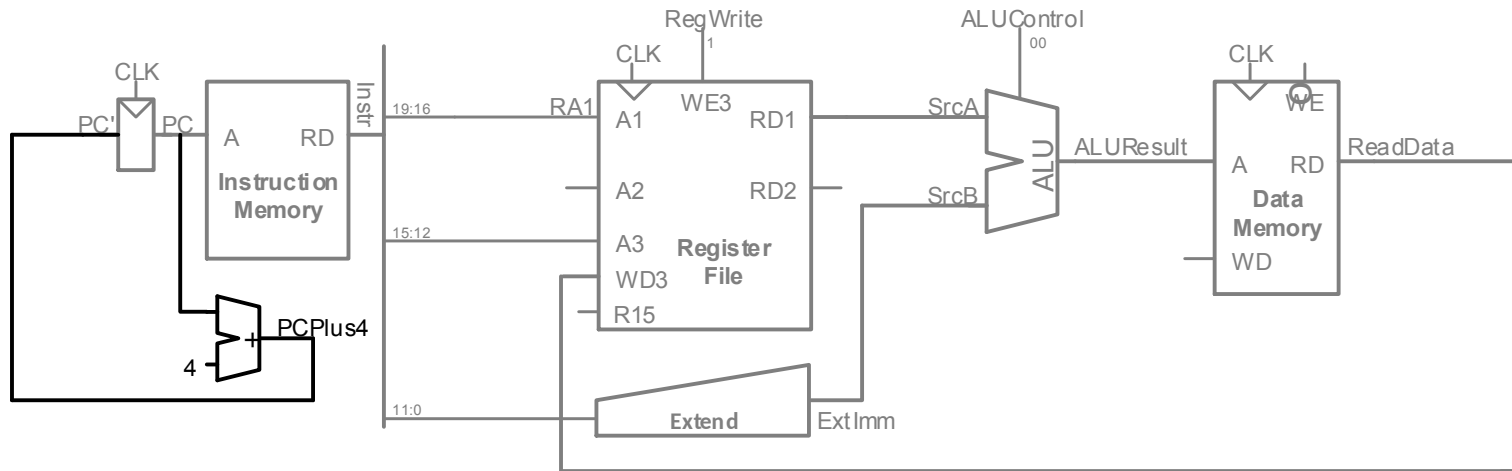
## STEP 6: Determine address of next instruction


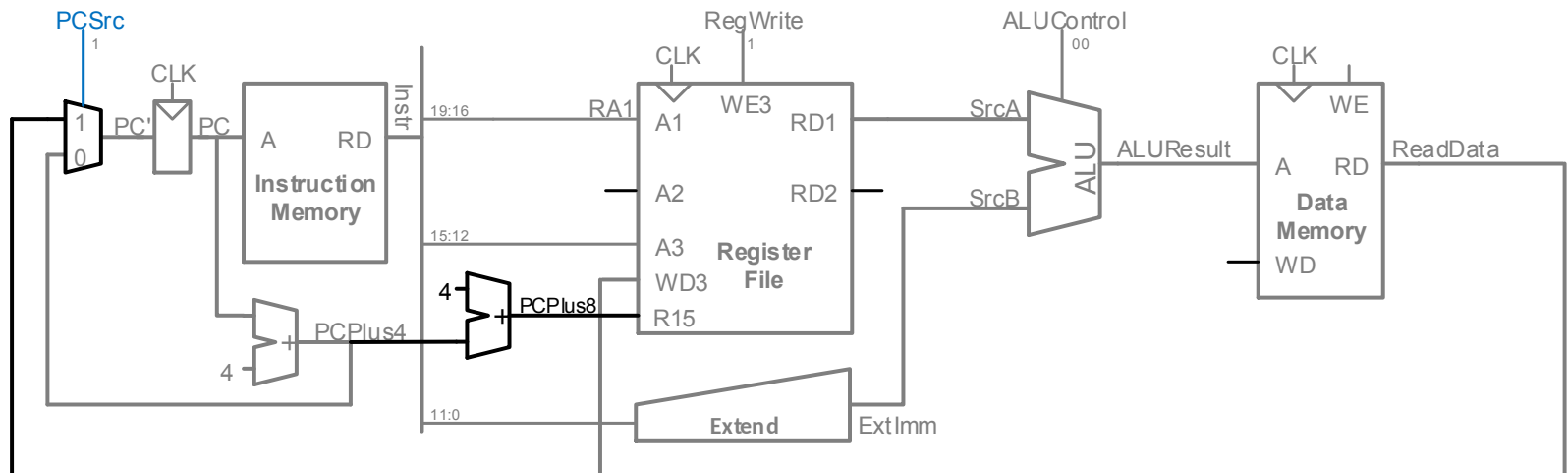
# Single-Cycle Datapath: Access to PC


PC can be source/destination of instruction


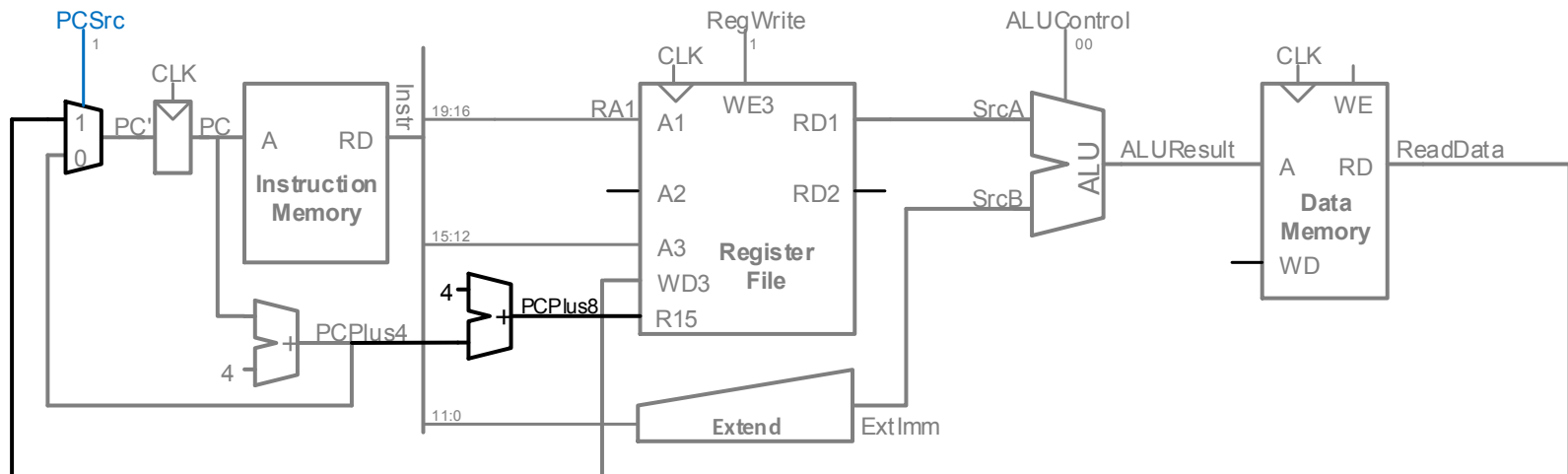
# Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction


- **Source:** R15 must be available in Register File
  - **PC** is read as the current **PC plus 8**


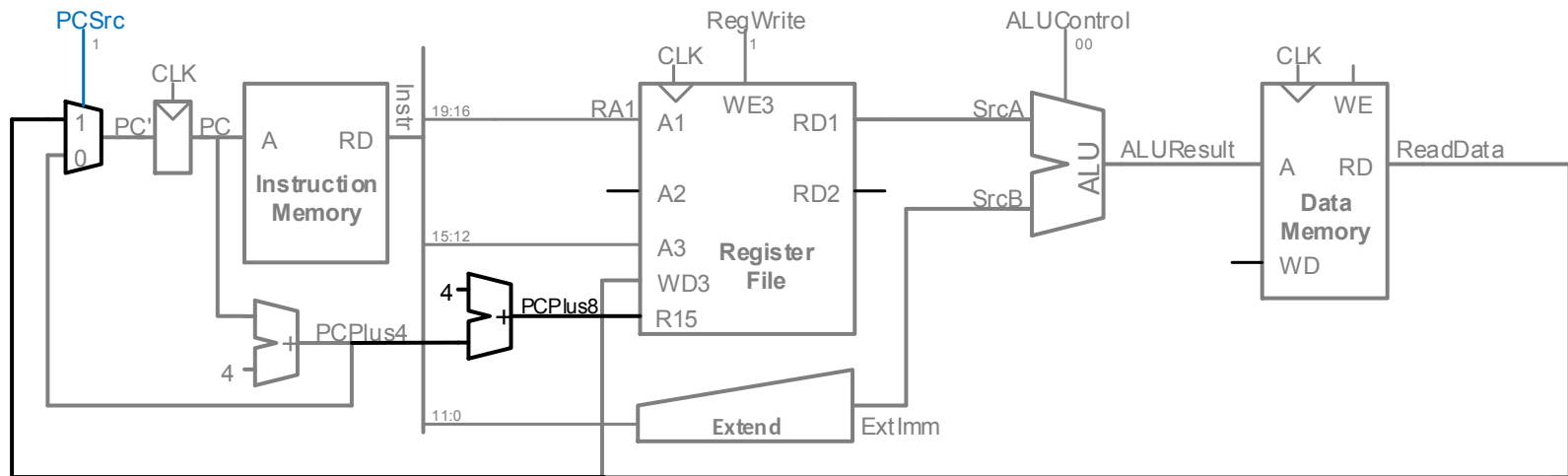
# Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction



- **Source:** R15 must be available in Register File
  - **PC** is read as the current **PC plus 8**
- **Destination:** Be able to write result to PC



# Single-Cycle Datapath: STR

## Expand datapath to handle STR:


- Write data in  $R_d$  to memory

 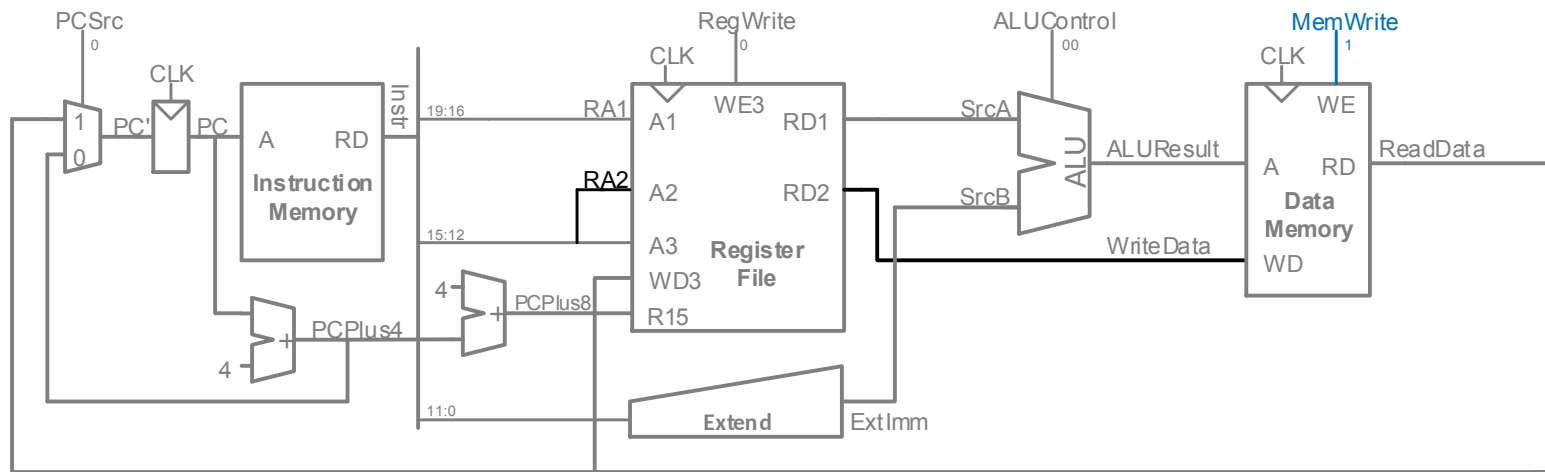

# Single-Cycle Datapath: Data-processing
 
## With **immediate** Src2:

- Read from  $R_n$  and  $Imm8$  ( $ImmSrc$  chooses the zero-extended  $Imm8$  instead of  $Imm12$ )
- Write  $ALUResult$  to register file
- Write to  $R_d$




**ADD  $R_d$ ,  $R_n$ , imm8**



# Single-Cycle Datapath: Data-processing
 
## With **immediate Src2**:

- Read from  $R_n$  and  $Imm8$  (*ImmSrc* chooses the zero-extended  $Imm8$  instead of  $Imm12$ )
- Write *ALUResult* to register file
- Write to  $R_d$




**ADD  $R_d$ ,  $R_n$ ,  $imm8$**



# Single-Cycle Datapath: Data-processing
 
## With **register Src2**:

- Read from  $R_n$  and  $R_m$  (instead of  $Imm8$ )
- Write *ALUResult* to register file
- Write to  $R_d$




**ADD  $R_d$ ,  $R_n$ ,  $R_m$**





# Single-Cycle Datapath: Data-processing

With **immediate Src2**:

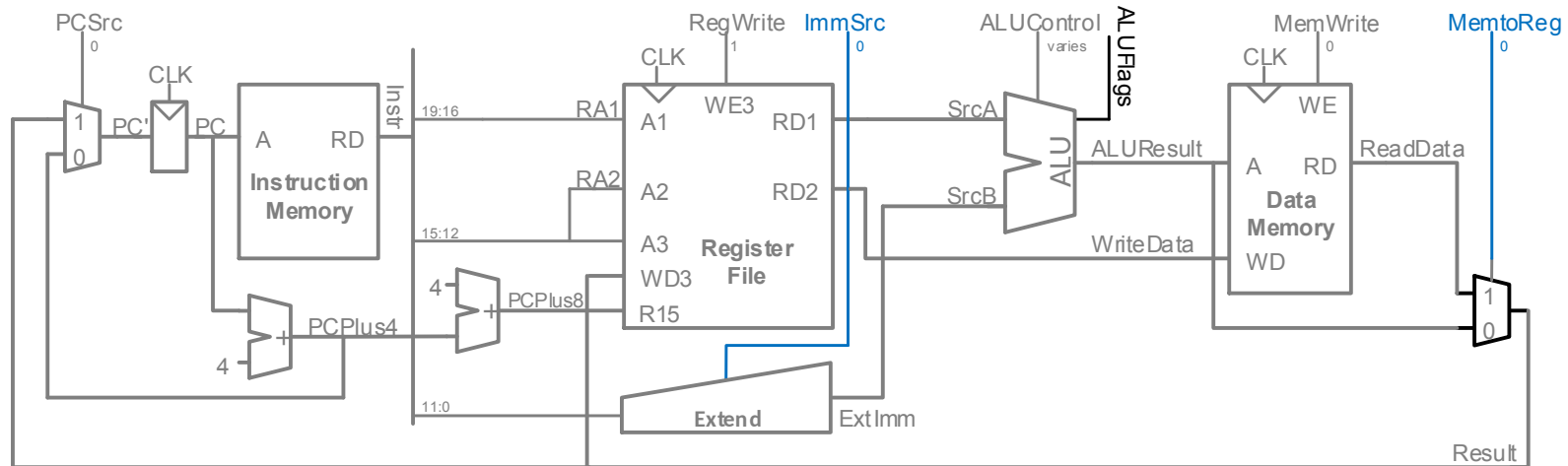


**ADD Rd, Rn, imm8**



# Single-Cycle Datapath: Data-processing
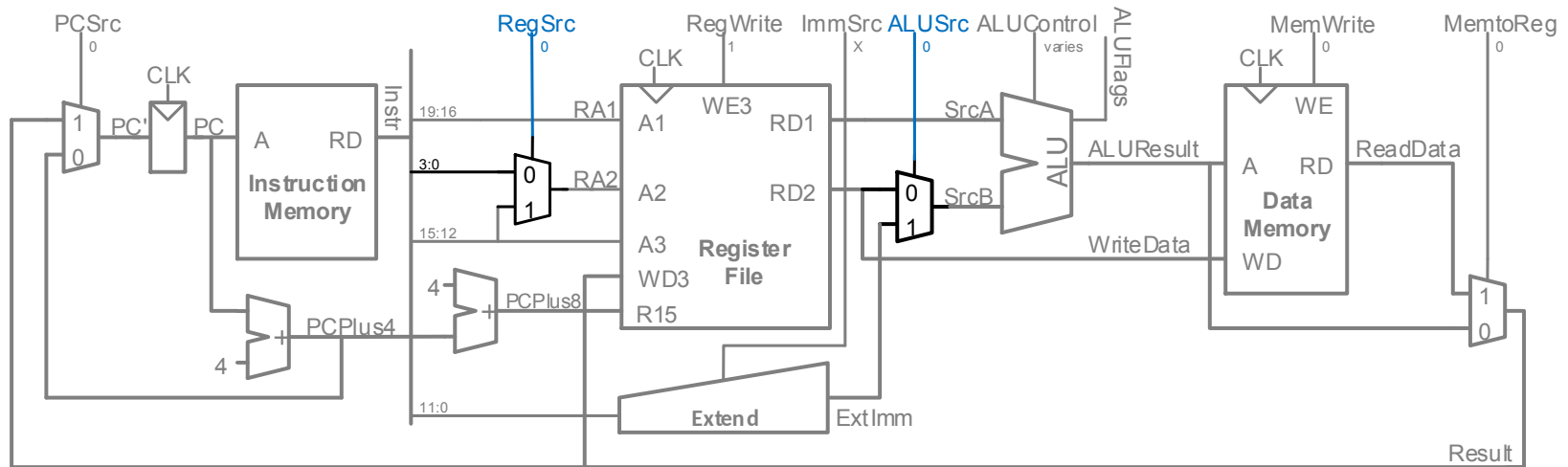
## With **register Src2**:

- Read from  $R_n$  and  $R_m$  (instead of  $Imm8$ )
- Write *ALUResult* to register file
- Write to  $R_d$



**ADD  $R_d, R_n, R_m$**




# Single-Cycle Datapath: B

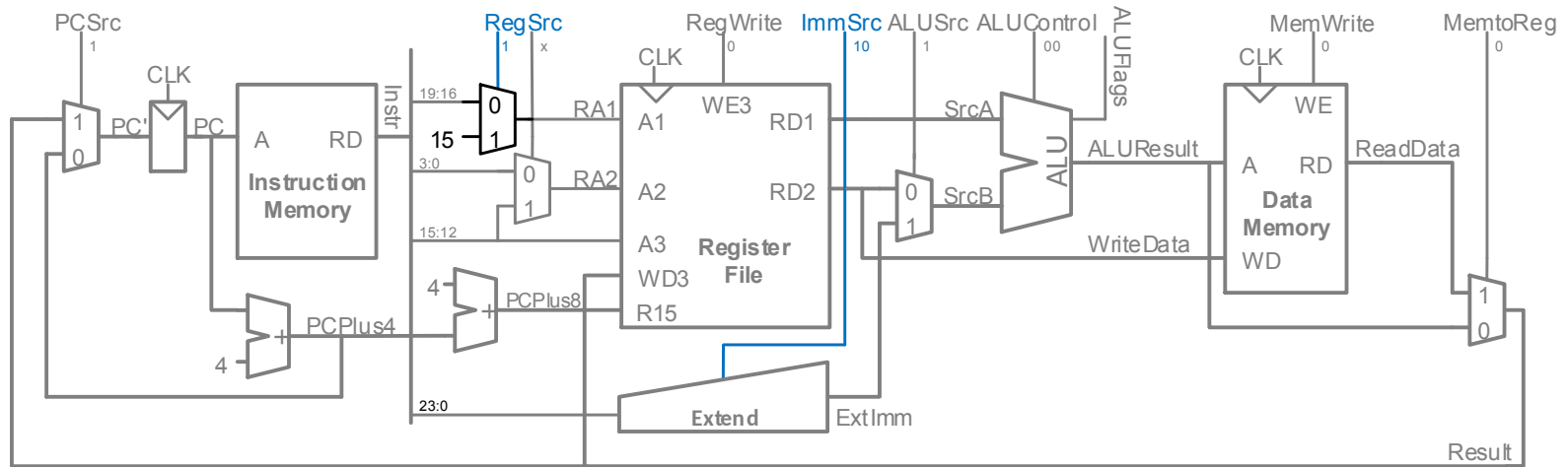
## Calculate branch target address:

$$\text{BTA} = (\text{ExtImm}) + (\text{PC} + 8)$$

$\text{ExtImm} = \text{Imm24} \ll 2$  and sign-extended




Branch

 

B Label




# Single-Cycle Datapath: ExtImm

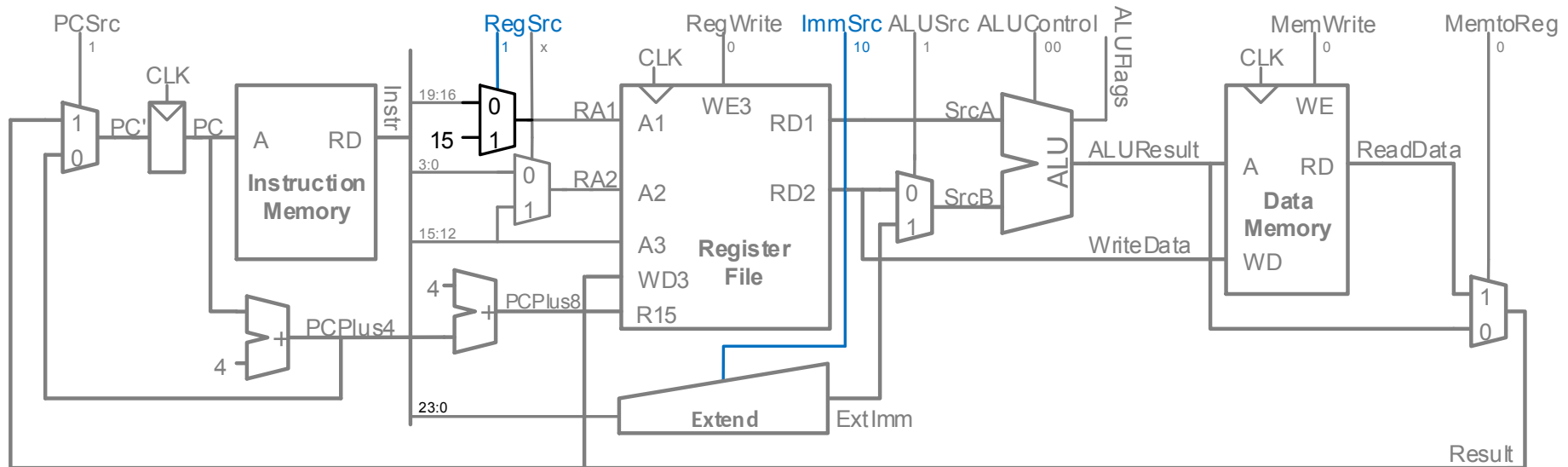


ImmSrc <sub>1:0</sub>	ExtImm	Description
00	{24'b0, Instr <sub>7:0</sub> }	Zero-extended <i>imm8</i>
01	{20'b0, Instr <sub>11:0</sub> }	Zero-extended <i>imm12</i>
10	{6{Instr <sub>23</sub> }, Instr <sub>23:0</sub> }	Sign-extended <i>imm24</i>




# Single-Cycle ARM Processor

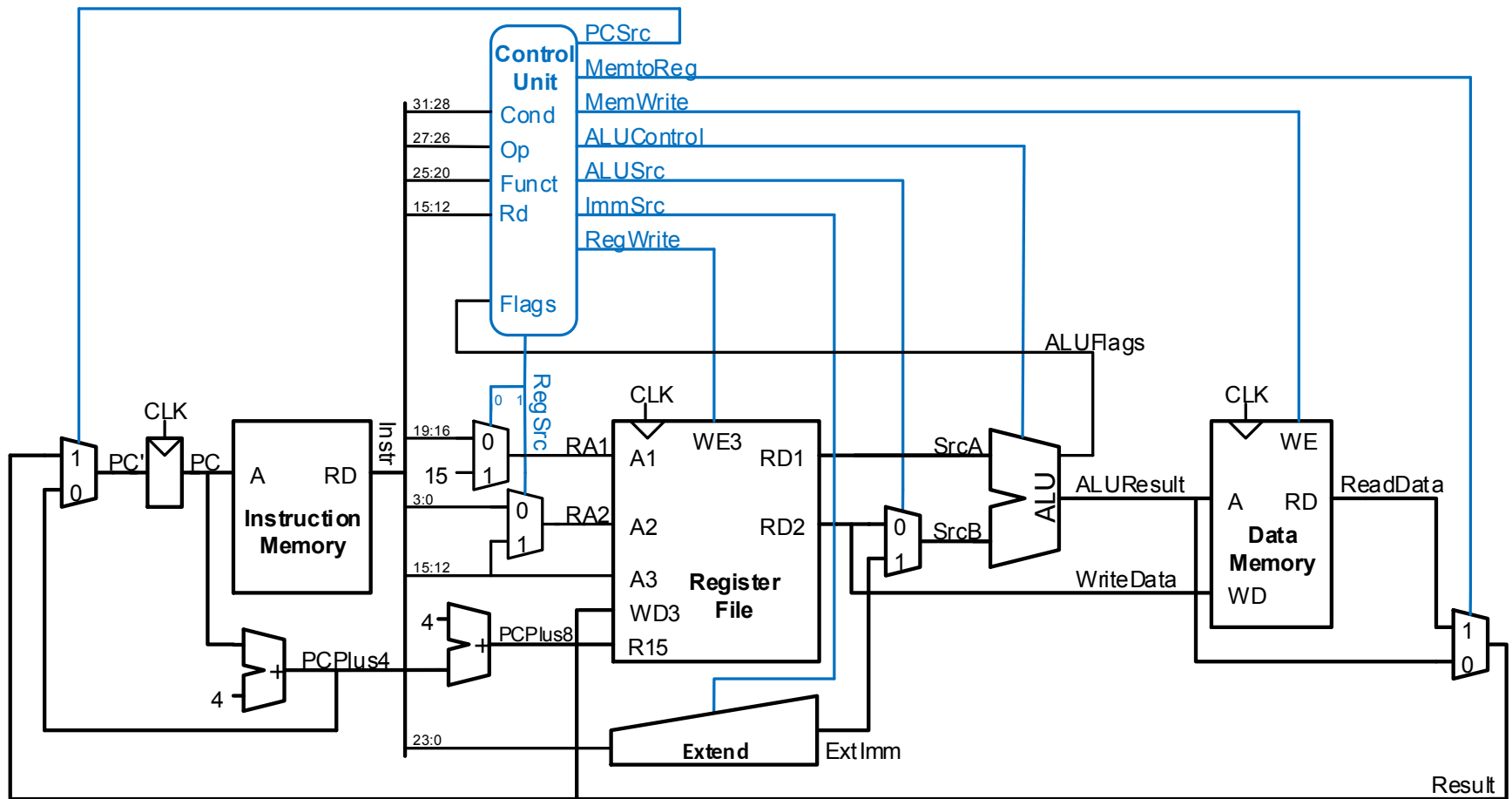


# Single-Cycle Control

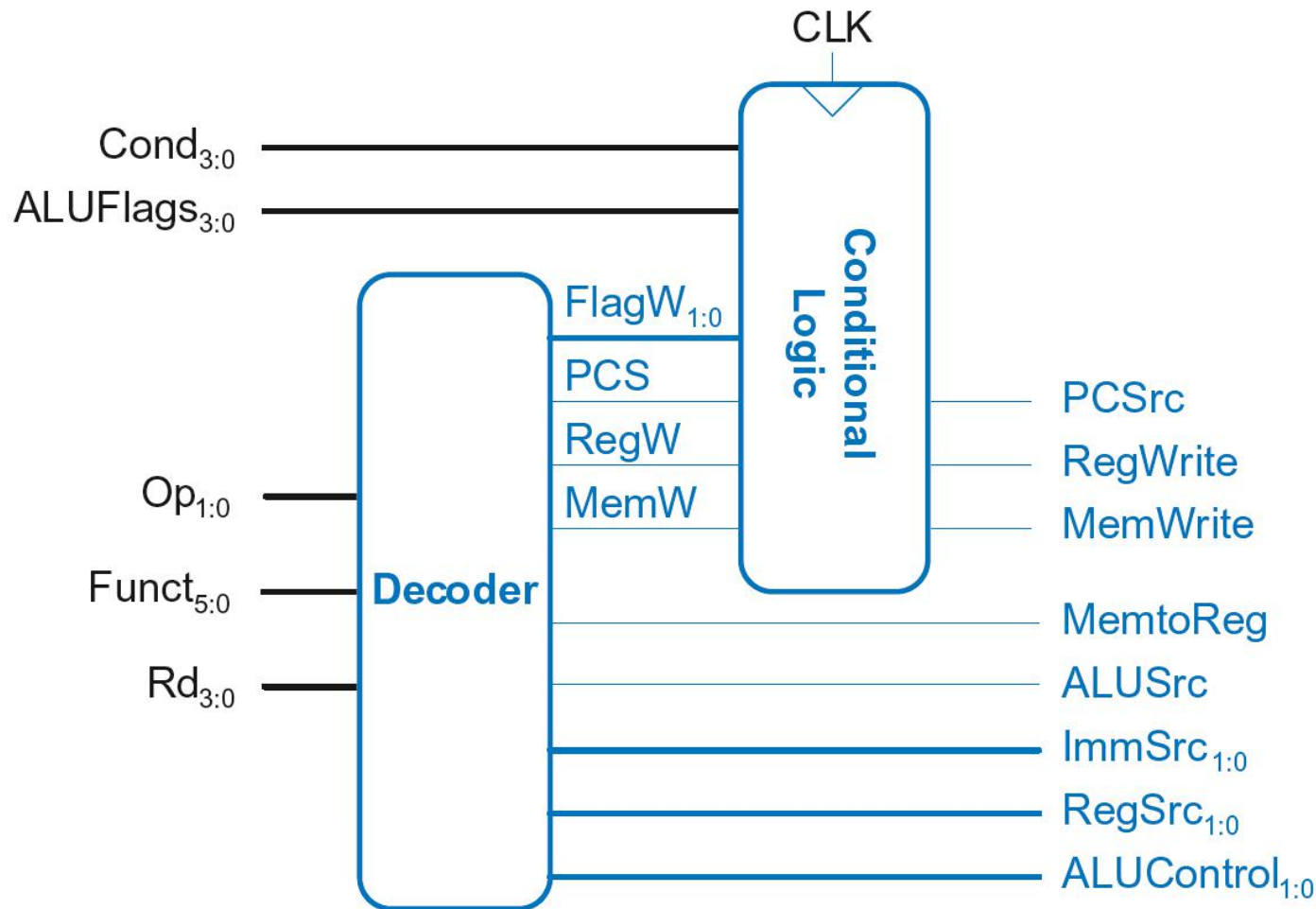

# Single-Cycle Control

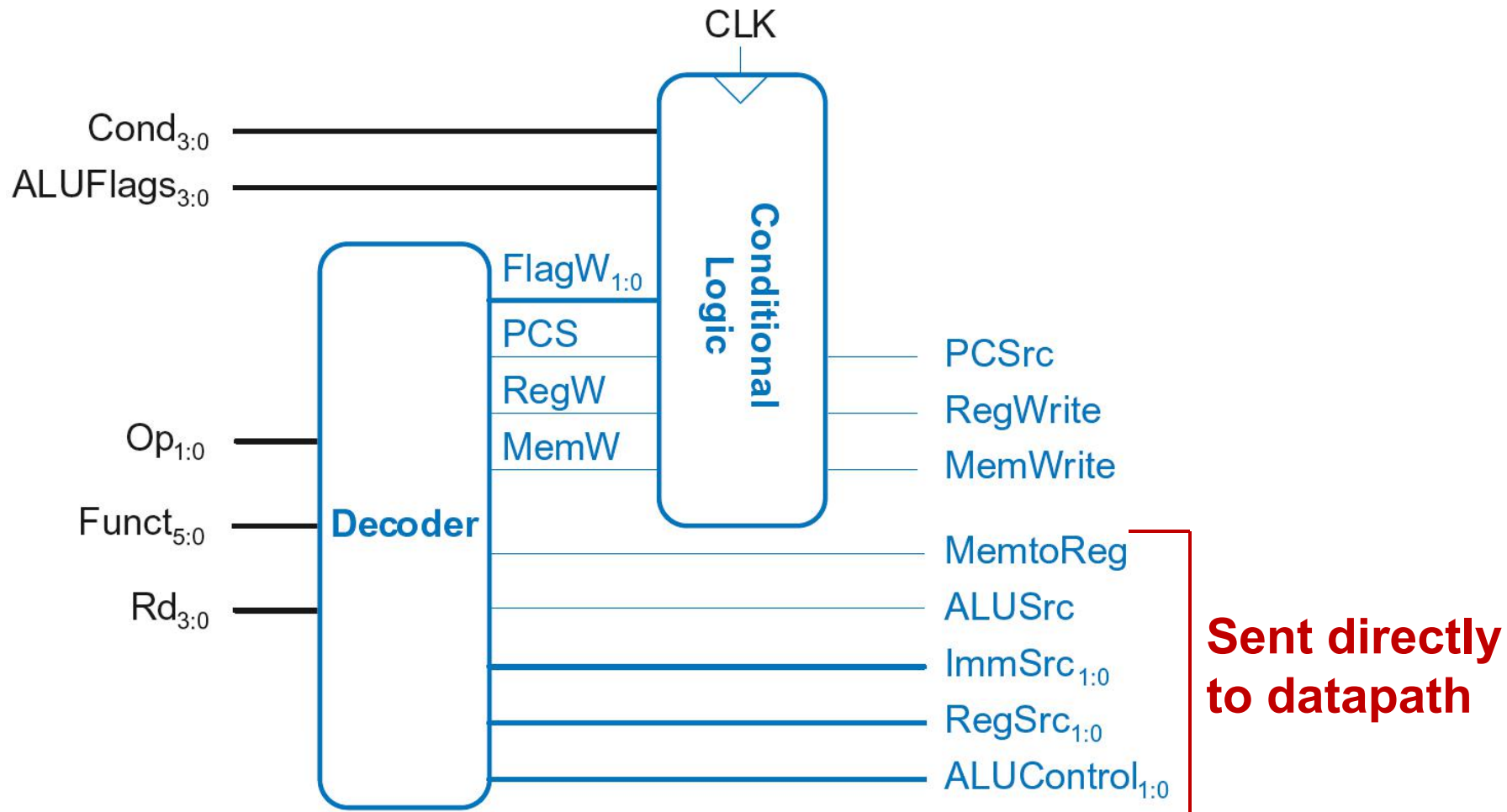


# Single-Cycle Control

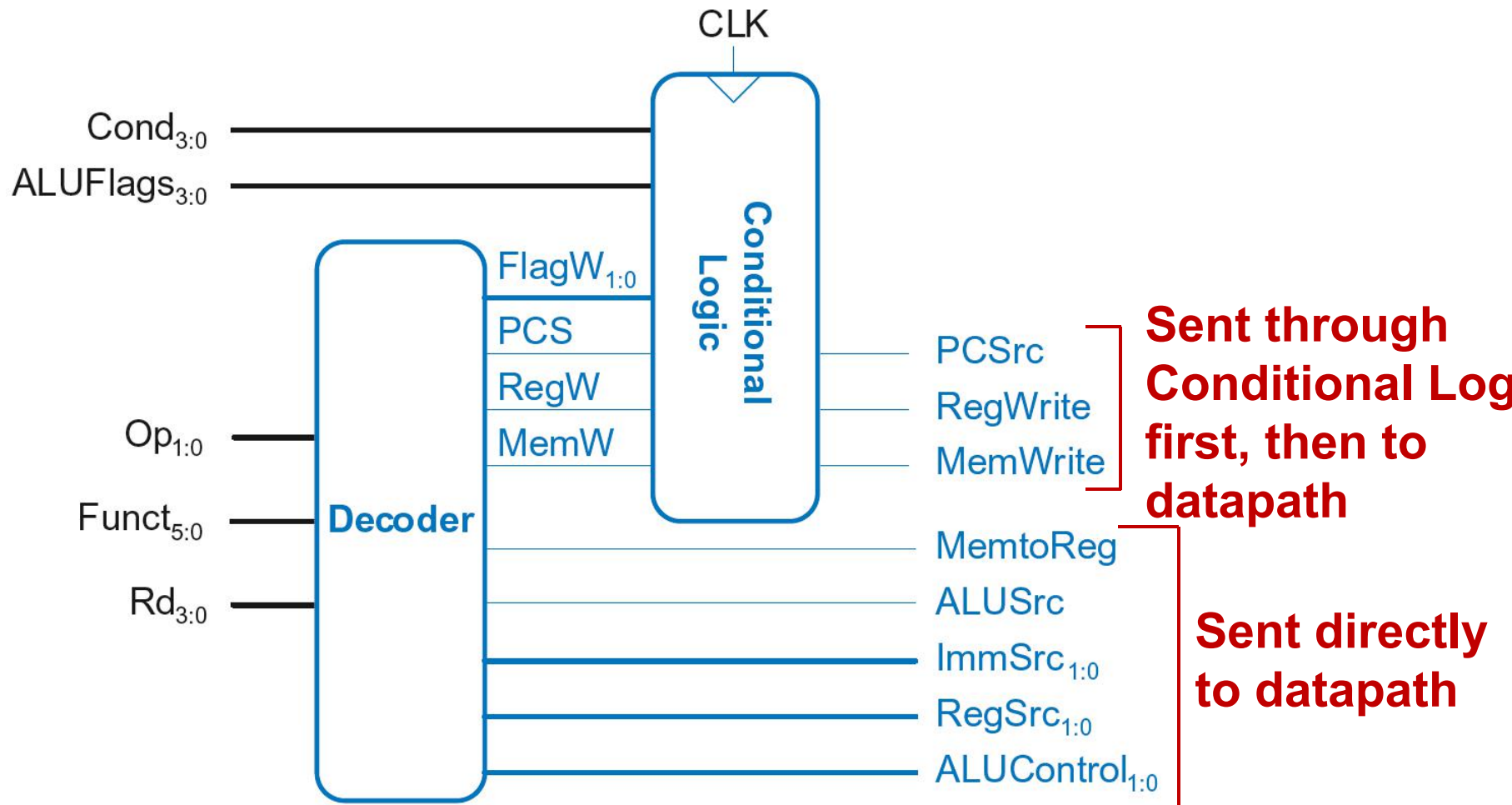



# Single-Cycle Control

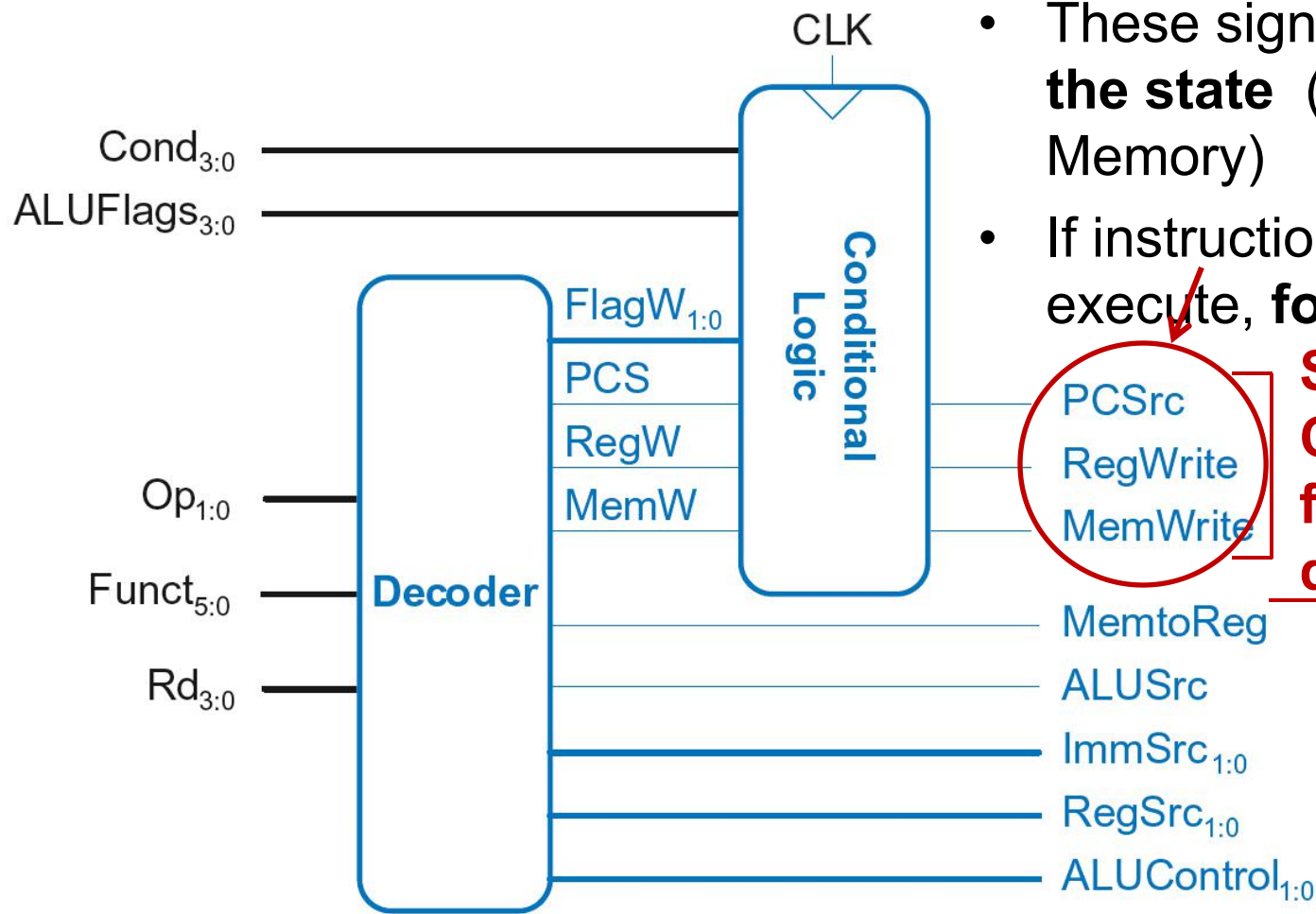

- These signals **change the state** (PC, RF, Memory)


- If instruction shouldn't execute, **forced to 0**

**Sent through Conditional Logic first, then to datapath**

**Sent directly to datapath**




# Single-Cycle Control

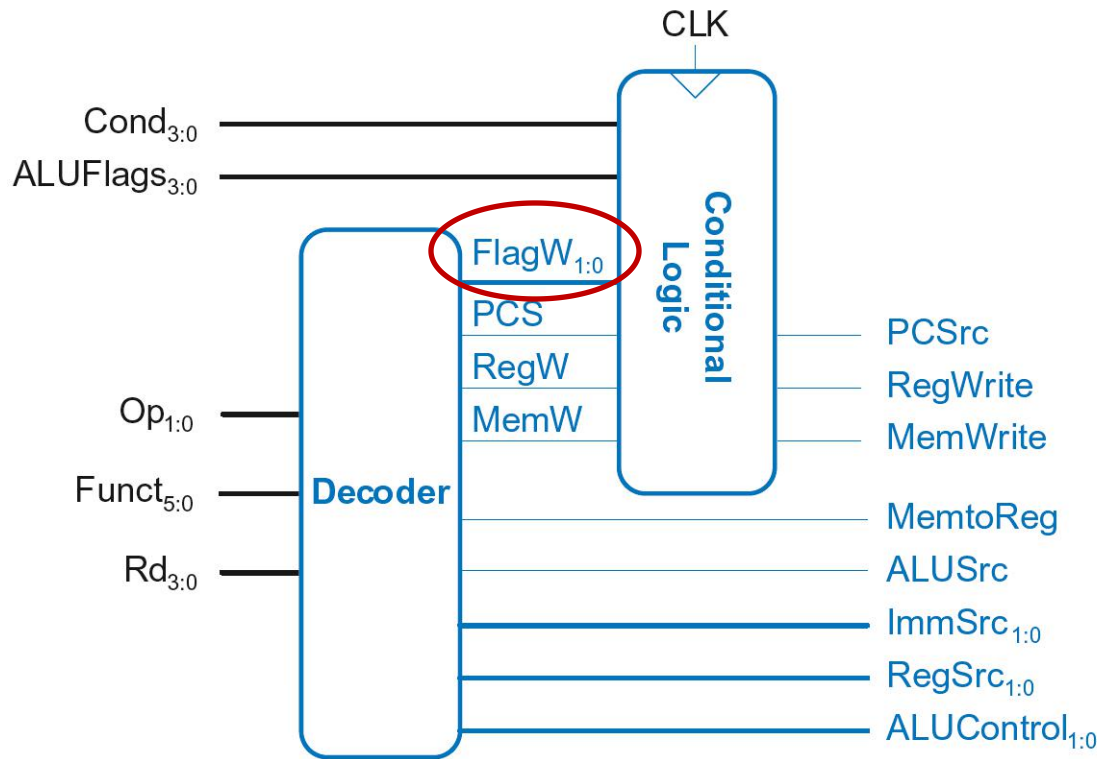

- ***FlagW<sub>1:0</sub>***: Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with  $S=1$ )




# Single-Cycle Control

 

- **$FlagW_{1:0}$** : Flag Write signal, asserted when  $ALUFlags$  should be saved (i.e., on instruction with  $S=1$ )
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags



# Single-Cycle Control

 


- **FlagW<sub>1:0</sub>**: Flag Write signal, asserted when **ALUFlags** should be saved (i.e., on instruction with S=1)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags
- So, two bits needed:

**FlagW<sub>1</sub> = 1: NZ**  
 saved (ALUFlags<sub>3:2</sub> saved)


**FlagW<sub>0</sub> = 1: CV**  
 saved (ALUFlags<sub>1:0</sub> saved)



# Single-Cycle Control

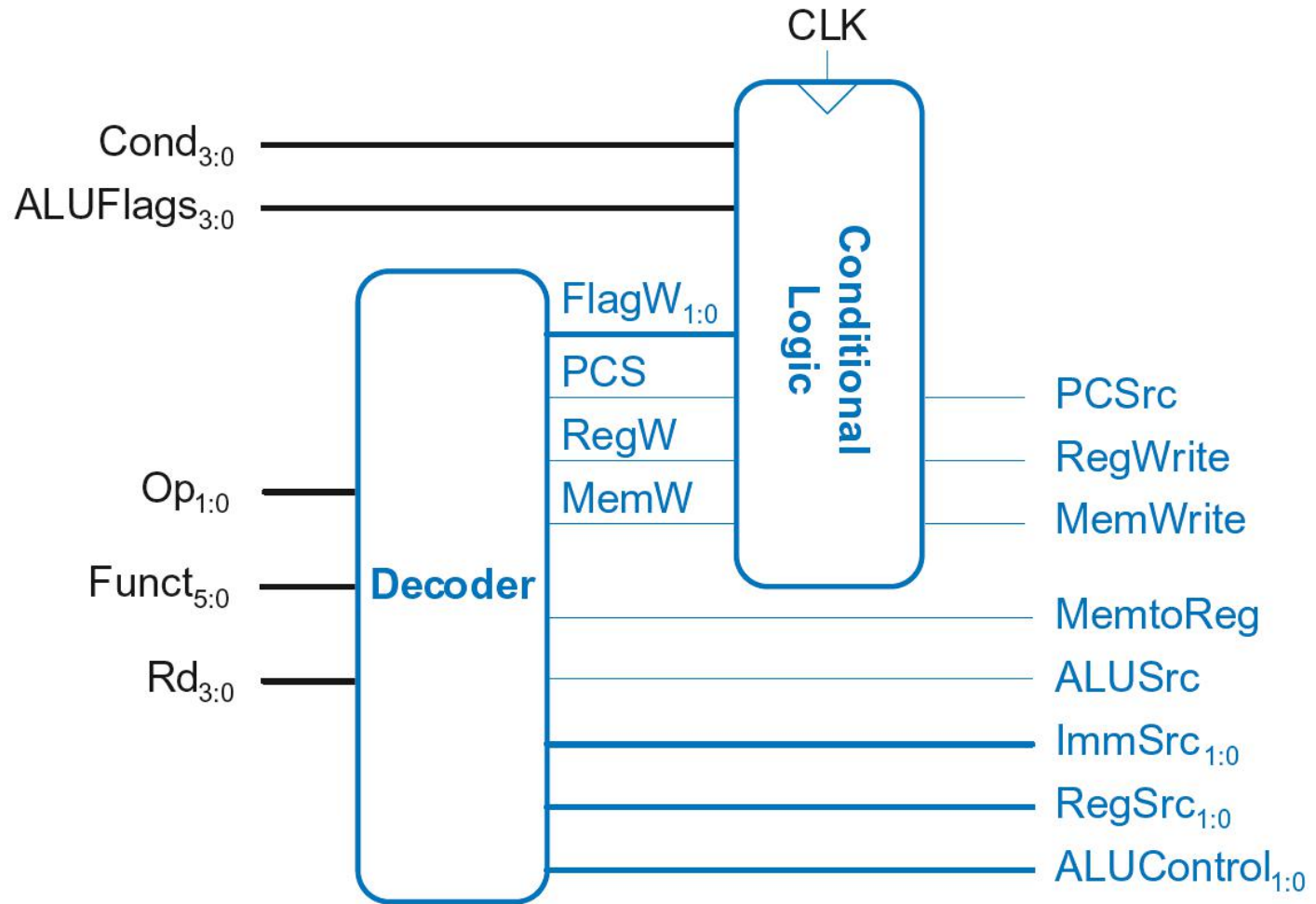


# Single-Cycle Control: Decoder

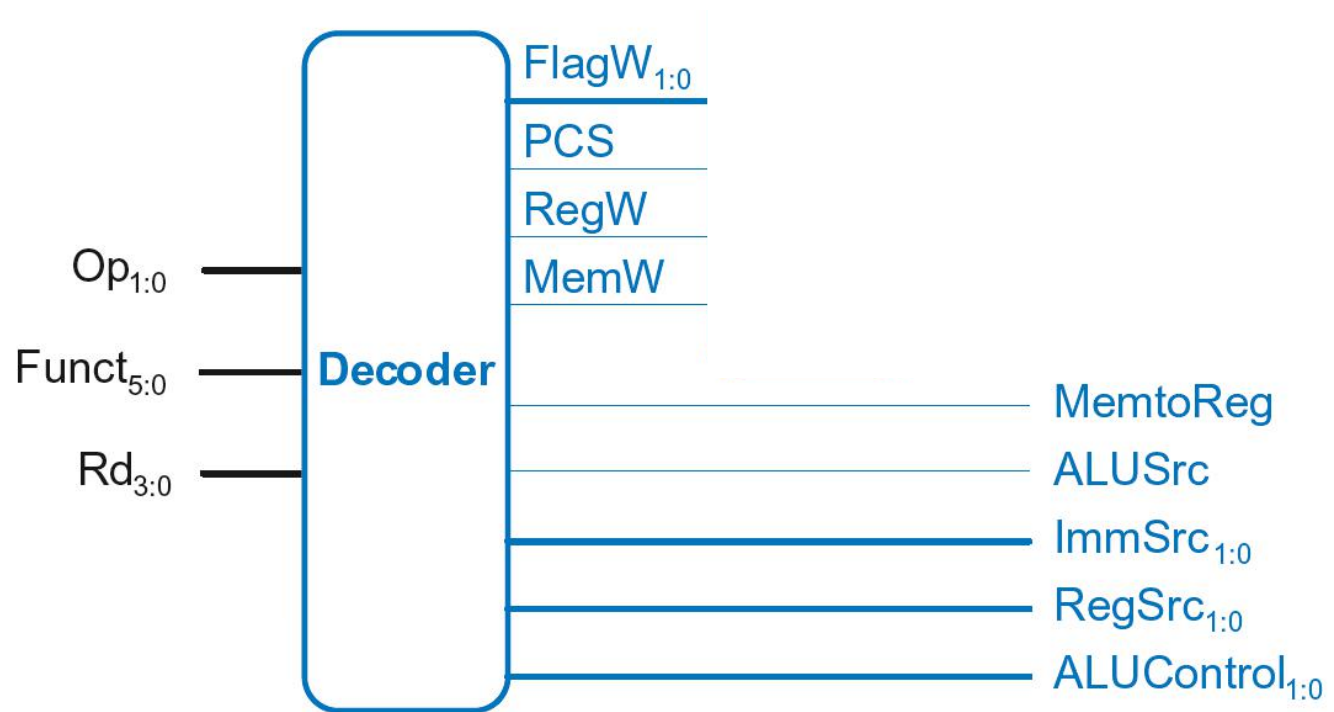

# Single-Cycle Control: Decoder

## Submodules:

- Main Decoder
- ALU Decoder
- PC Logic

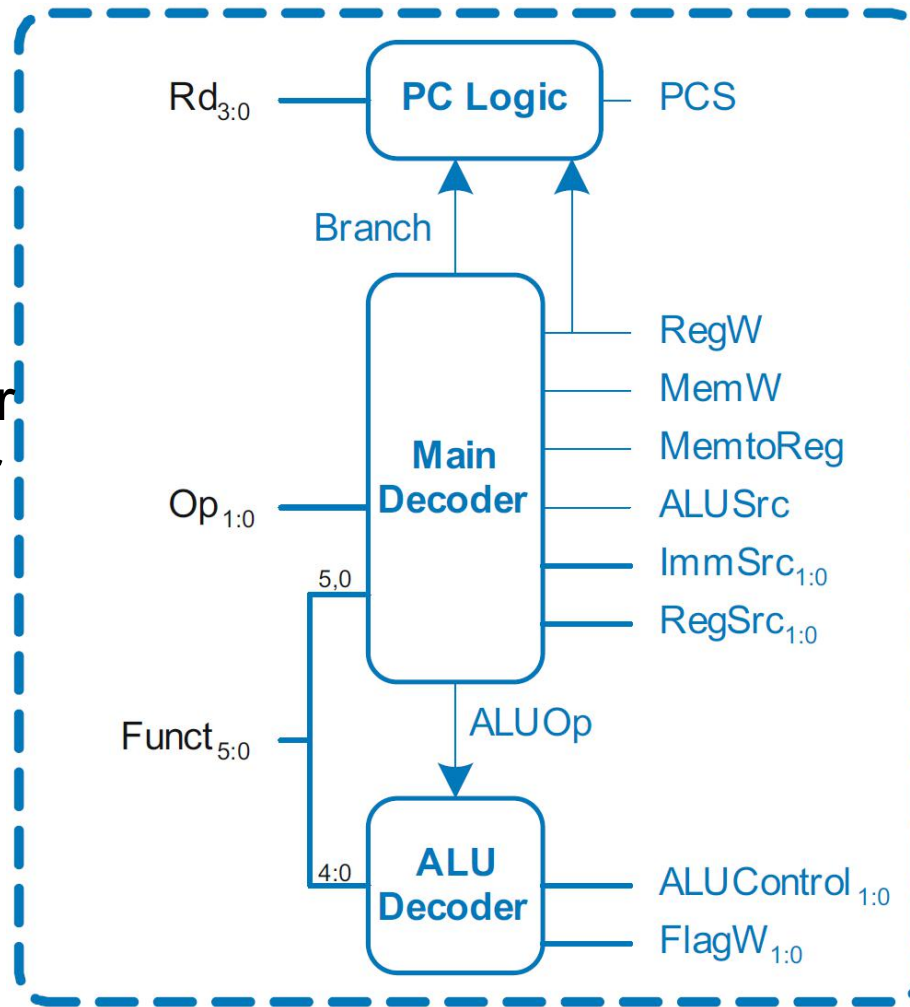




# Single-Cycle Control: Decoder
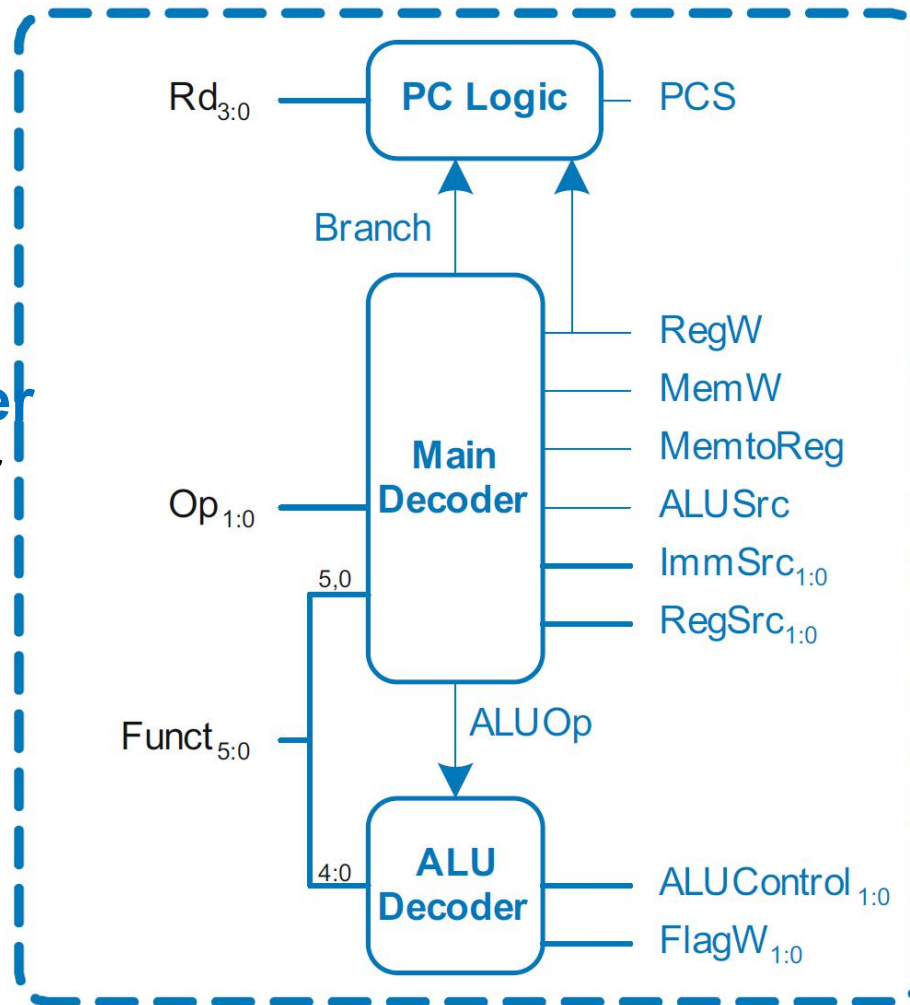
## Submodules:

- **Main Decoder**
- ALU Decoder
- PC Logic





# Control Unit: Main Decoder


Op	Funct <sub>5</sub>	Funct <sub>0</sub>	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
11	X	X	B	1	0	0	1	10	0	X1	0



# Single-Cycle Control: Decoder

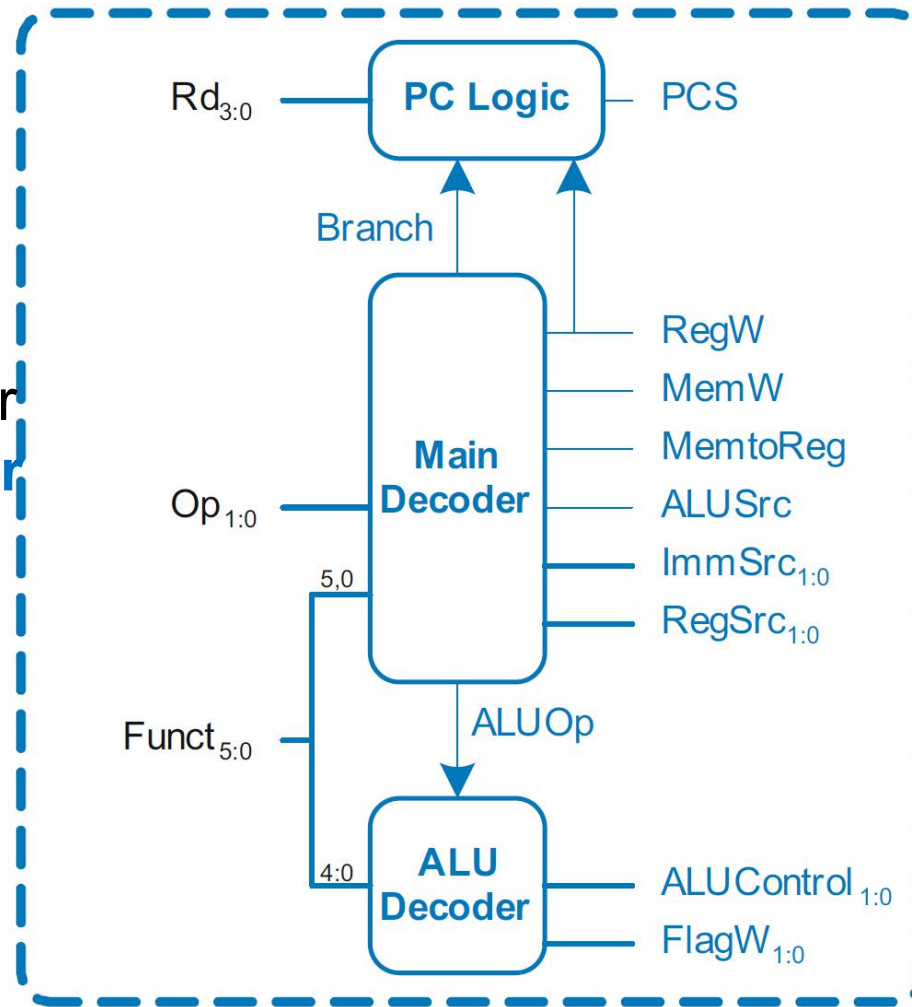
## Submodules:


- Main Decoder
- **ALU Decoder**
- PC Logic



# Review: ALU

ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

 


 

# Single-Cycle Control: Decoder
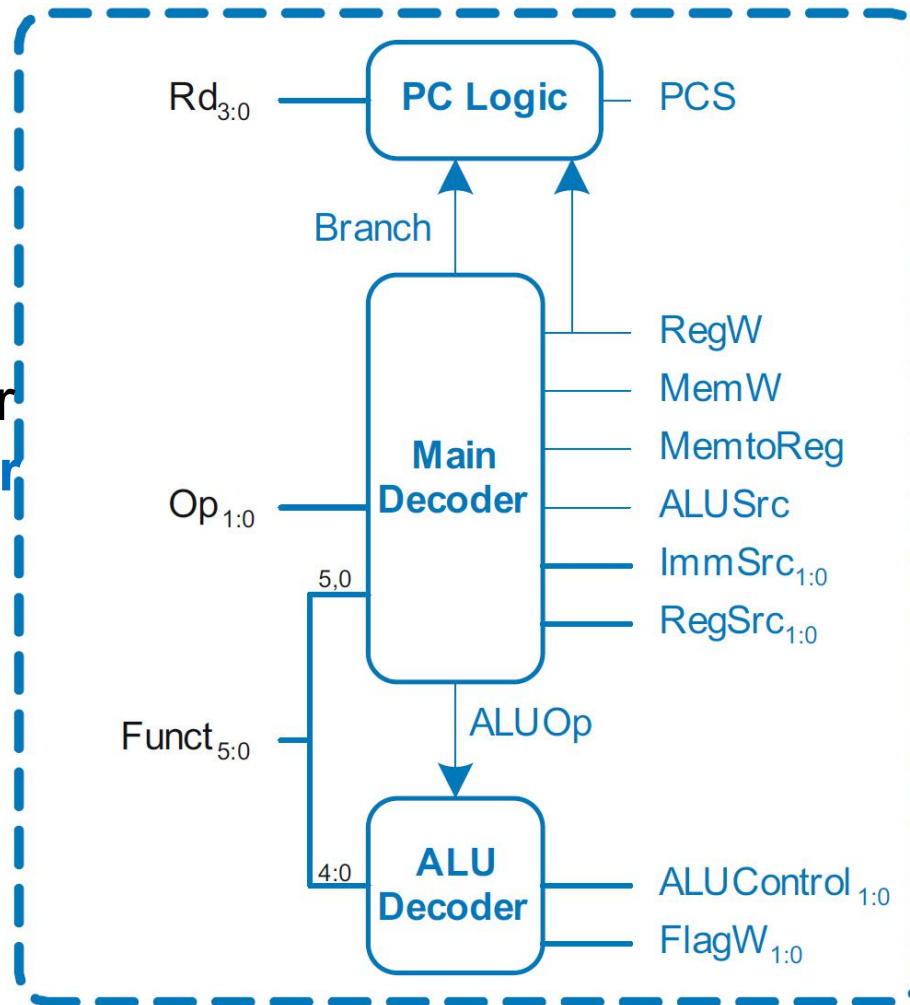
## Submodules:

- Main Decoder
- **ALU Decoder**
- PC Logic



# Control Unit: ALU Decoder

ALUOp	Funct <sub>4:1</sub> (cmd)	Funct <sub>0</sub> (S)	Type	ALUControl <sub>1:0</sub>	FlagW <sub>1:0</sub>
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10


- **FlagW<sub>1</sub>** = 1: NZ (*Flags*<sub>3:2</sub>) should be saved
- **FlagW<sub>0</sub>** = 1: CV (*Flags*<sub>1:0</sub>) should be saved



# Single-Cycle Control: Decoder

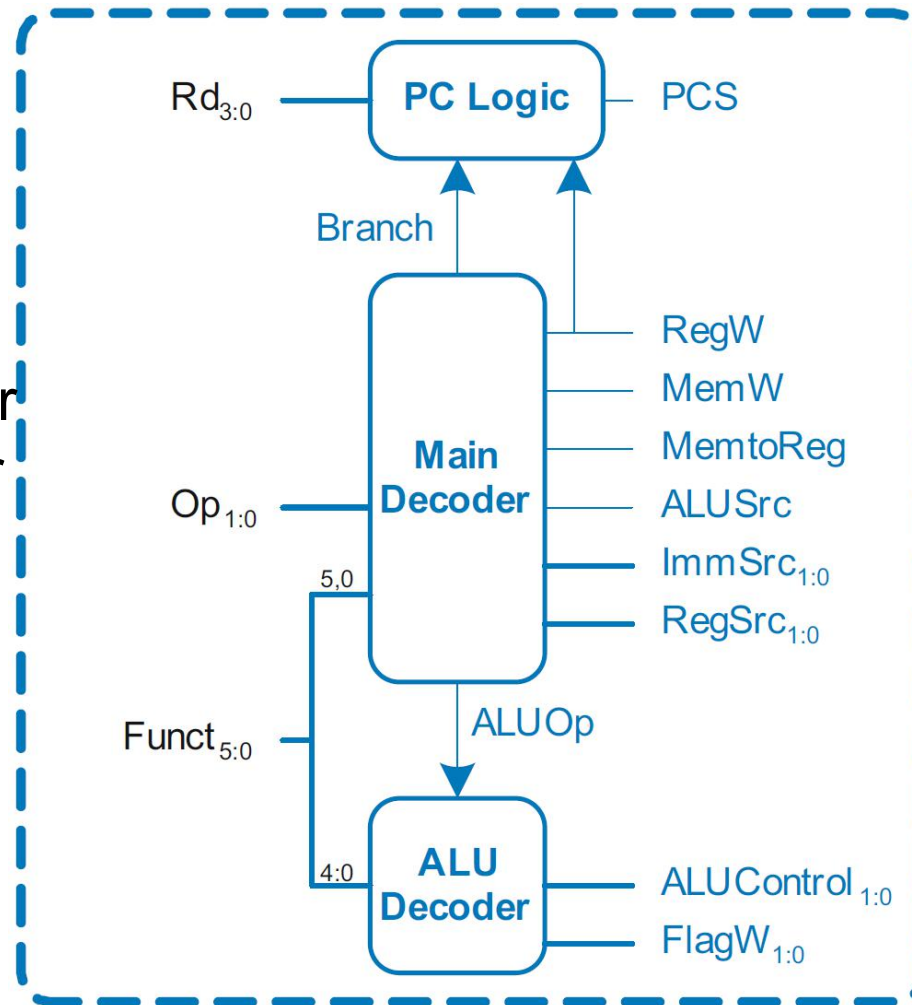
## Submodules:

- Main Decoder
- ALU Decoder
- **PC Logic**



# Single-Cycle Control: PC Logic

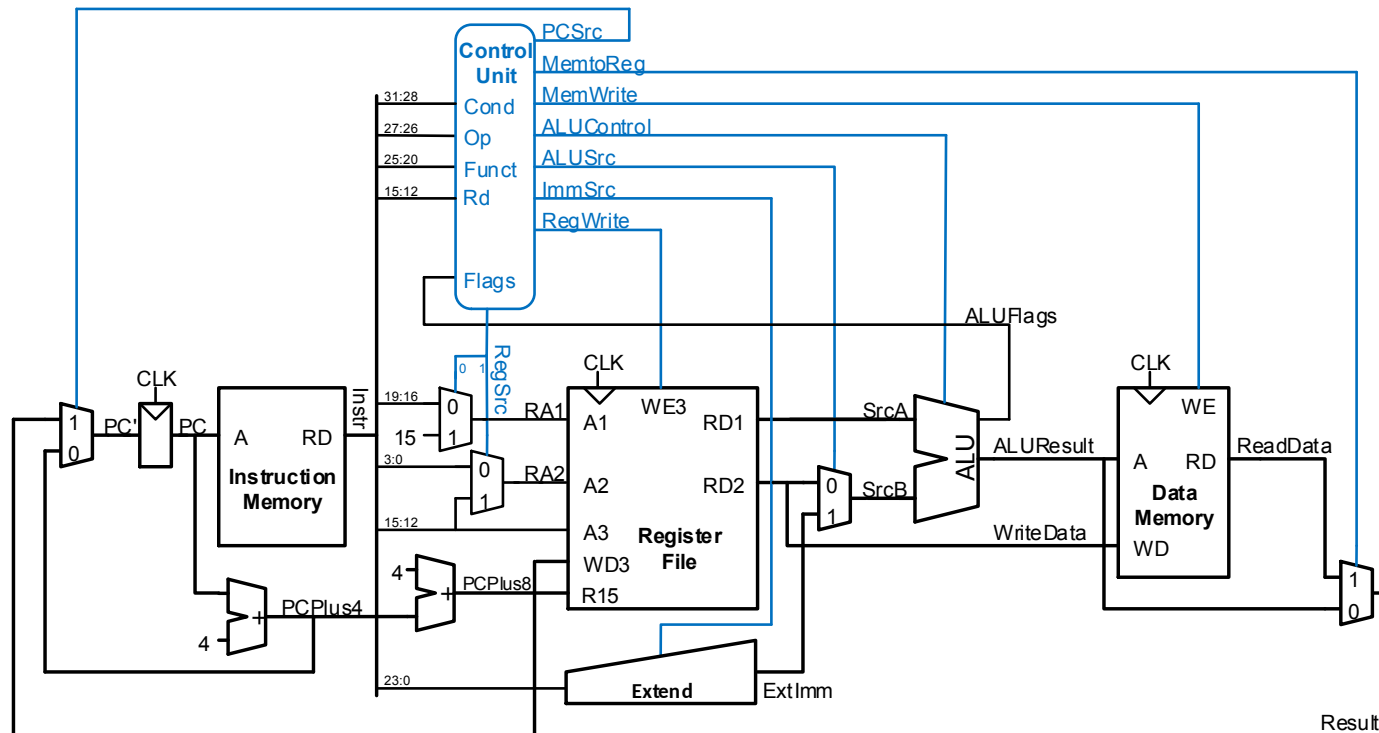**$PCS = 1$  if PC is written by an instruction or branch (B):  $PCS = ((Rd == 15) \& RegW) \mid Branch$**



**If instruction is executed:  $PCSrc = PCS$**


**Else**

**$PCSrc = 0$  (i.e.,  $PC = PC + 4$ )**







# Single-Cycle Control

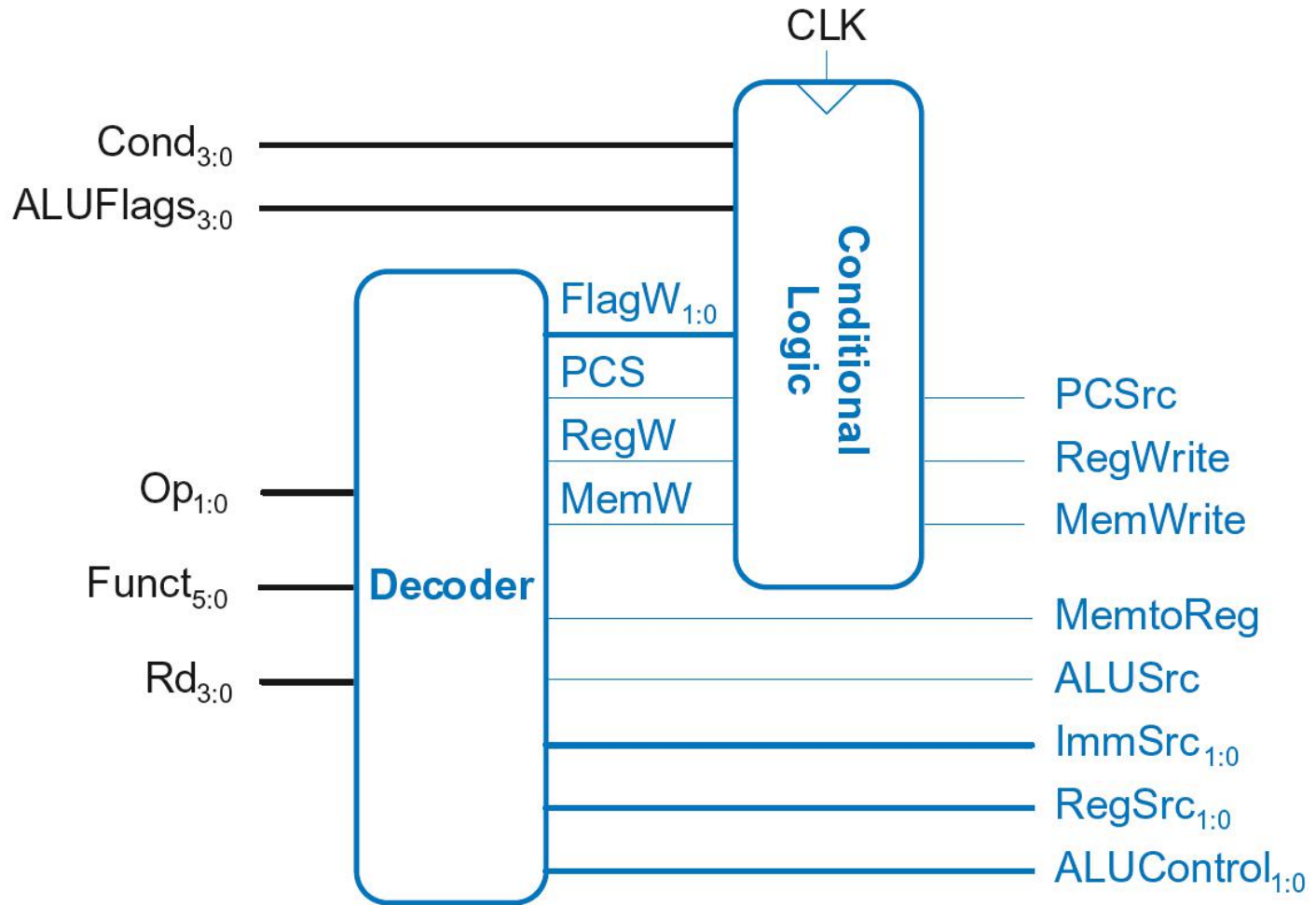

# Single-Cycle Control: Cond. Logic

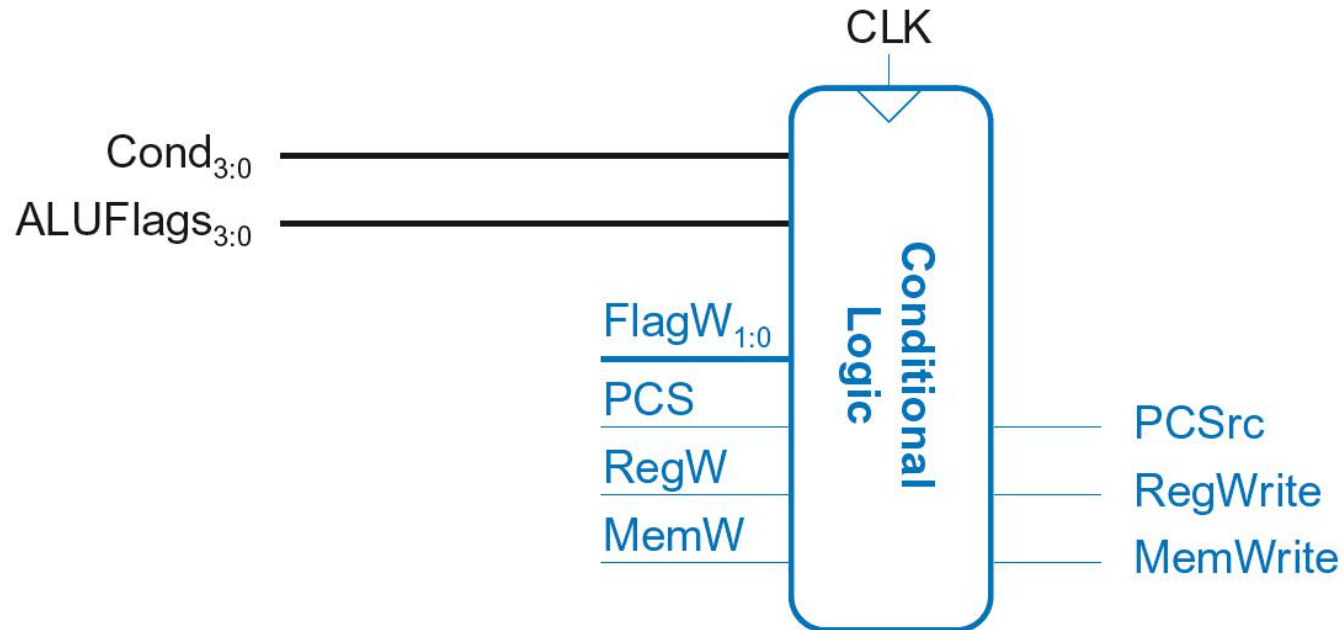

# Conditional Logic

 


## Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags<sub>3:0</sub>)



# Conditional Logic

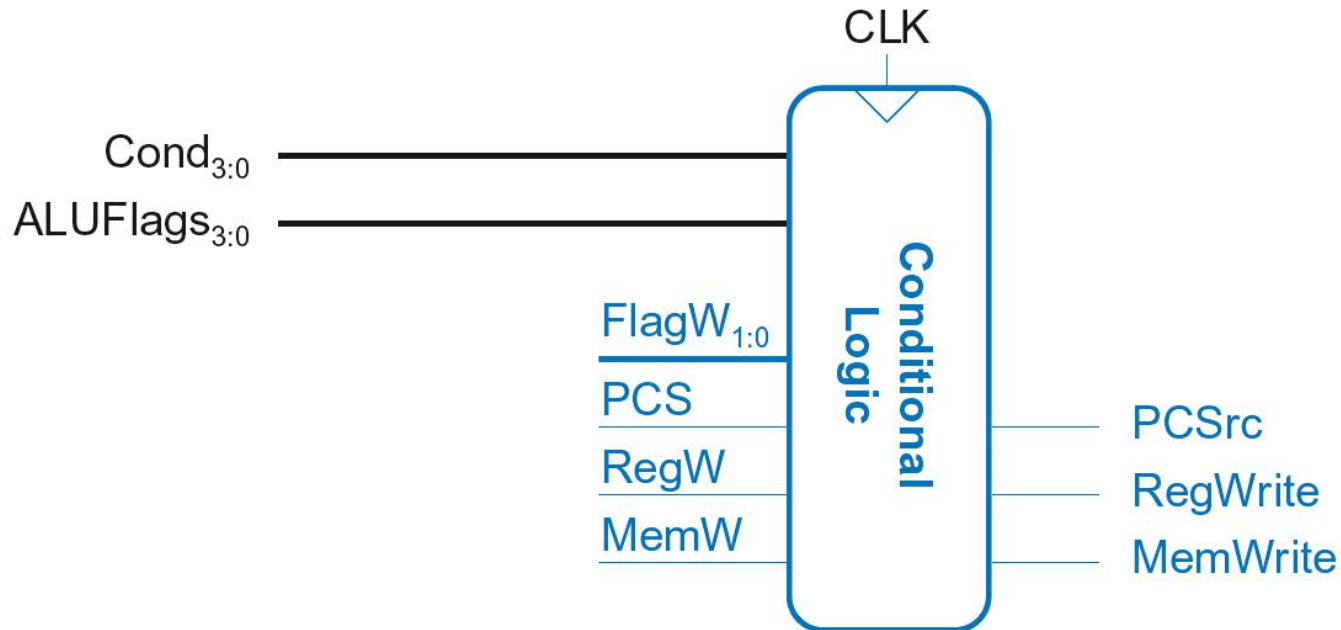


## Function:

1. Check if instruction should execute (if not, force **PCSrc**, **RegWrite**, and **MemWrite** to 0)
2. Possibly update Status Register (Flags<sub>3:0</sub>)




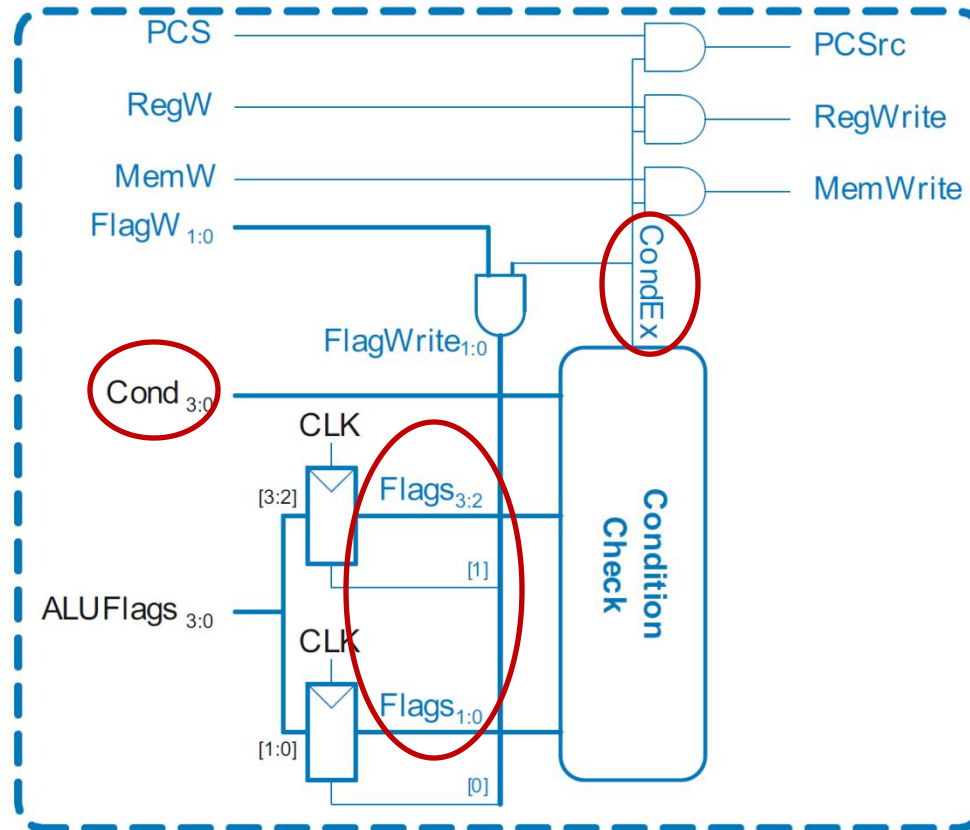
# Conditional Logic: Conditional Execution




Depending on condition mnemonic (**Cond**<sub>3:0</sub>) and condition flags (**Flags**<sub>3:0</sub>) the instruction is executed (**CondEx** = 1)



# Conditional Logic: Conditional Execution

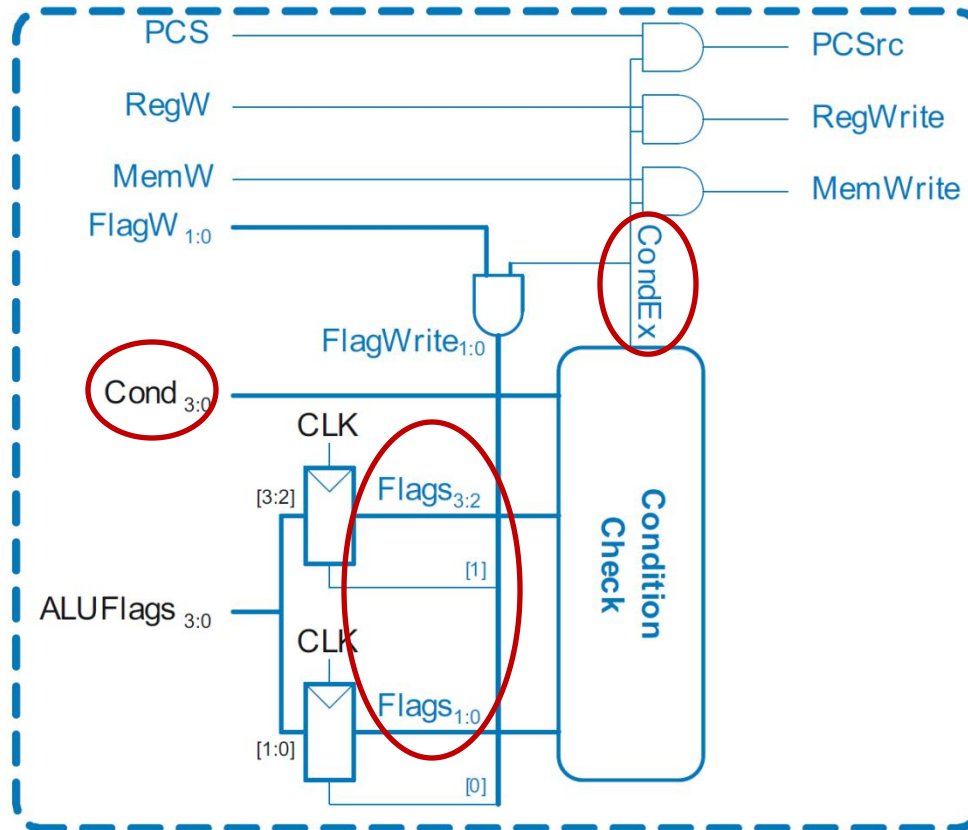**Flags<sub>3:0</sub>** is the **status register**



Depending on condition mnemonic (**Cond<sub>3:0</sub>**) and condition flags (**Flags<sub>3:0</sub>**) the instruction is executed (**CondEx = 1**)



# Review: Condition Mnemonics


Cond <sub>3:</sub> 0	Mnemonic	Name	CondEx
0000	EQ	Equal	$Z$
0001	NE	Not equal	$\bar{Z}$
0010	CS / HS	Carry set / Unsigned higher or same	$C$
0011	CC / LO	Carry clear / Unsigned lower	$\bar{C}$
0100	MI	Minus / Negative	$N$
0101	PL	Plus / Positive of zero	$\bar{N}$
0110	VS	Overflow / Overflow set	$V$
0111	VC	No overflow / Overflow clear	$\bar{V}$
1000	HI	Unsigned higher	$\bar{Z}C$
1001	LS	Unsigned lower or same	$Z OR \bar{C}$
1010	GE	Signed greater than or equal	$\overline{N \oplus V}$
1011	LT	Signed less than	$N \oplus V$
1100	GT	Signed greater than	$\bar{Z}(\overline{N \oplus V})$
1101	LE	Signed less than or equal	$Z OR (N \oplus V)$
1110	AL (or none)	Always / unconditional	ignored





# Conditional Logic: Conditional Execution

**Flags<sub>3:0</sub> =**  
NZCV

 

**Example:**

AND R1, R2, R3


**Cond<sub>3:0</sub> = 1110** (unconditional)

=> **CondEx = 1**



# Conditional Logic: Conditional Execution

**Flags<sub>3:0</sub> =**  
NZCV

 

**Example:**

EOREQ R5, R6, R7


**Cond<sub>3:0</sub>=0000 (EQ):** if **Flags<sub>3:2</sub>=0100**

=>

**CondEx = 1**



# Conditional Logic

 


## Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. **Possibly update Status Register (Flags<sub>3:0</sub>)**



# Conditional Logic: Update (Set) Flags


**Flags<sub>3:0</sub> =**  
NZCV

 

**Flags<sub>3:0</sub> updated** (with ALUFlags<sub>3:0</sub>) if:

- **FlagW** is 1 (i.e., the instruction's S-bit is 1)  
AND
- **CondEx** is 1 (the instruction should be executed)

# Conditional Logic: Update (Set) Flags

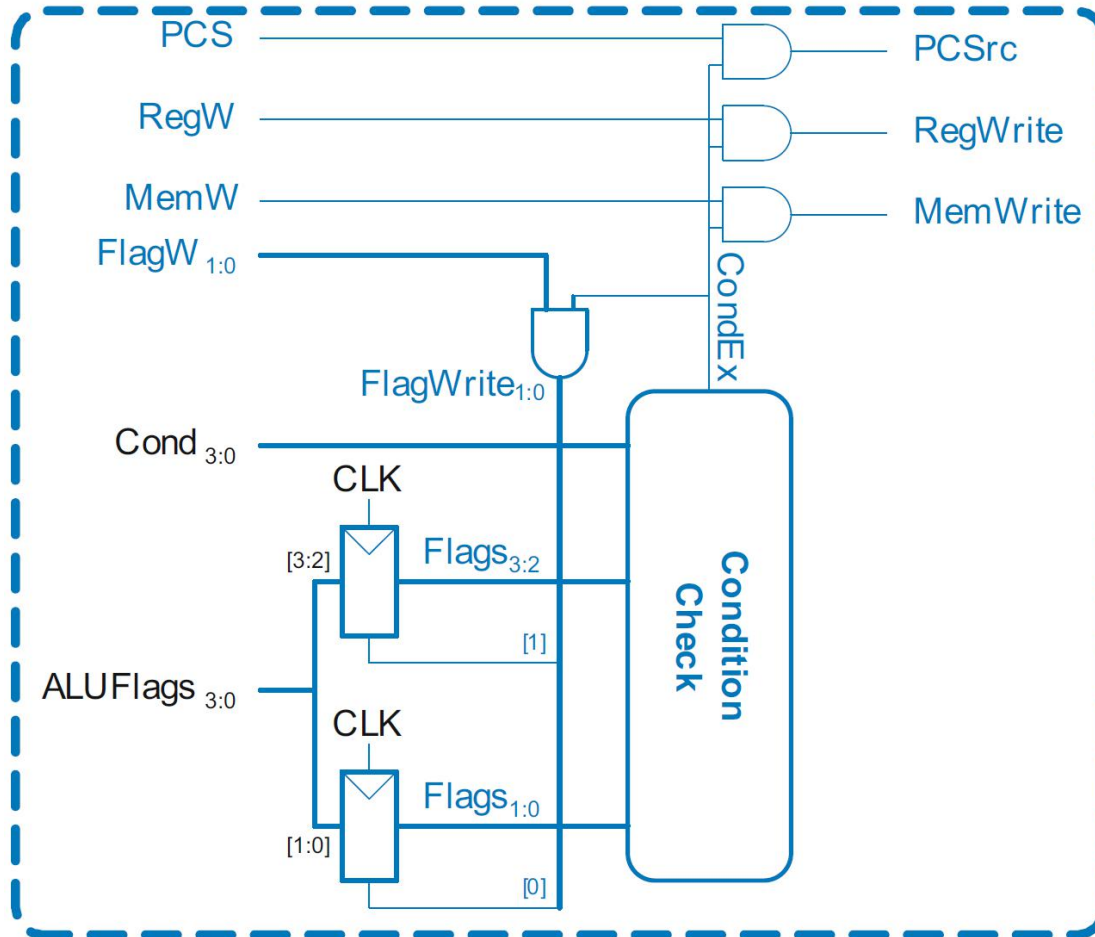

## Recall:

- ADD, SUB  
update **all** Flags
- AND, OR update  
**NZ only**
- So Flags status  
register has two  
write enables:  
**FlagW<sub>1:0</sub>**



# Review: ALU Decoder


ALUOp	Func <sub>4:1</sub> (cmd)	Func <sub>0</sub> (S)	Type	ALUControl <sub>1:0</sub>	FlagW <sub>1:0</sub>
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

- **FlagW<sub>1</sub>** = 1: NZ (*Flags*<sub>3:2</sub>) should be saved
- **FlagW<sub>0</sub>** = 1: CV (*Flags*<sub>1:0</sub>) should be saved



# Conditional Logic: Update (Set) Flags

All Flags  
updated

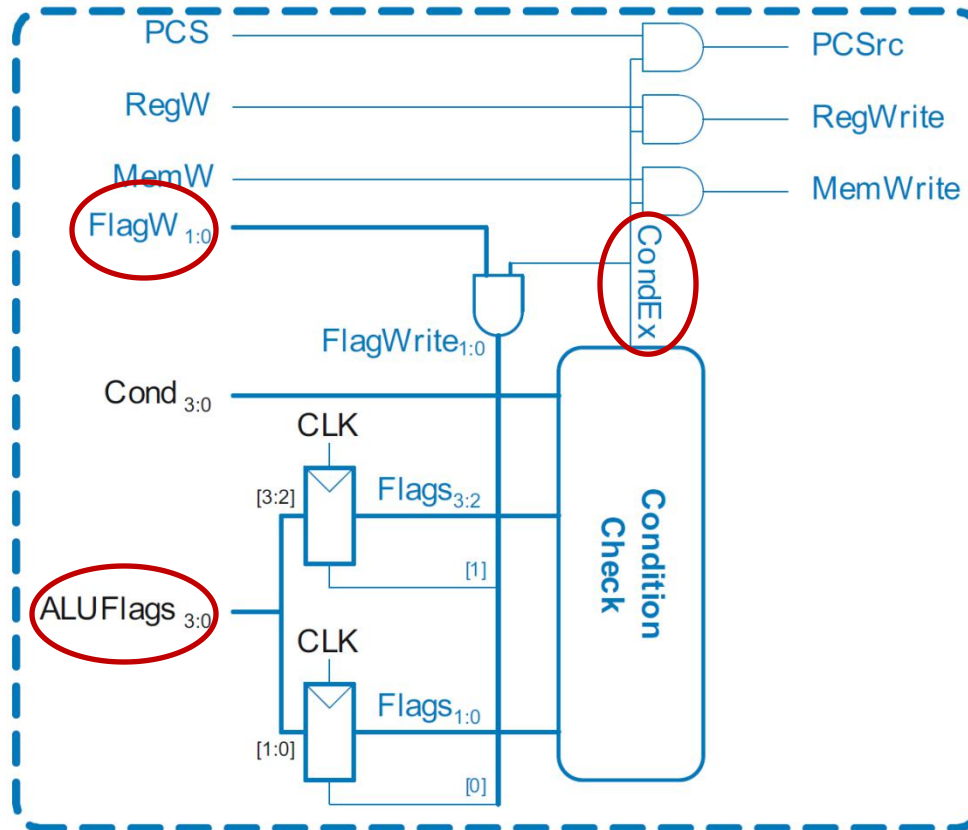

**Example:** SUBS R5, R6, R7


**FlagW**<sub>1:0</sub> = 11 AND **CondEx** = 1 (unconditional) => **FlagWrite**<sub>1:0</sub> = 11



# Conditional Logic: Update (Set) Flags

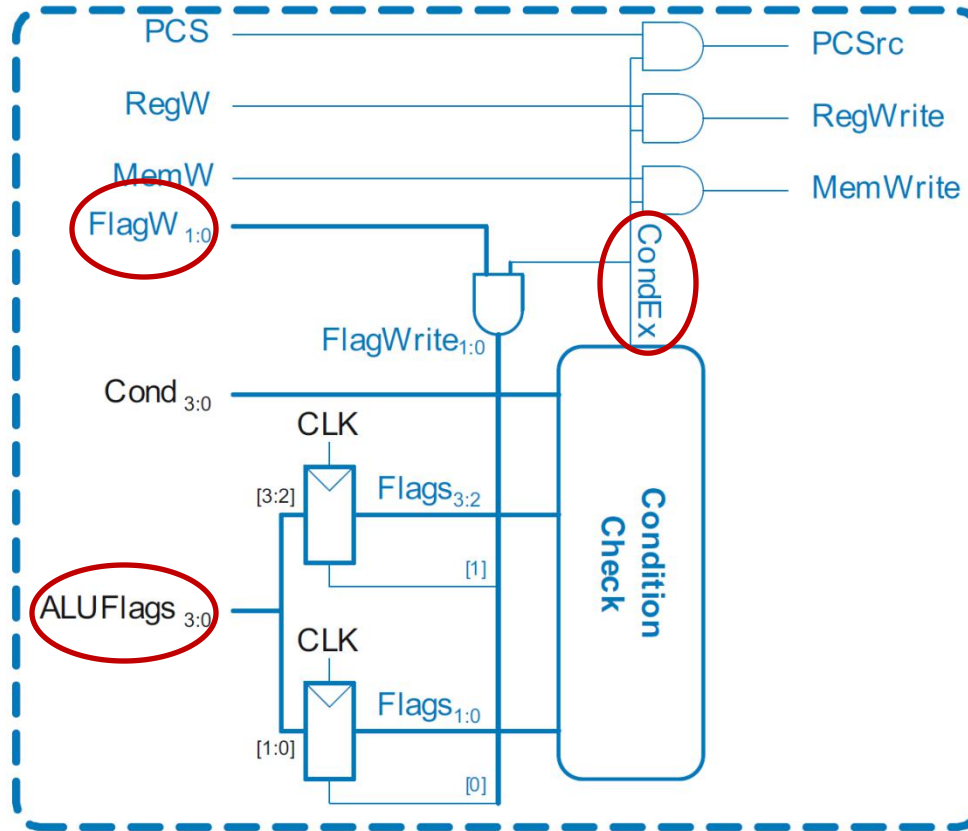**Flags<sub>3:0</sub> = NZCV**

- Only **Flags<sub>3:2</sub>** updated
- i.e., only **NZ** Flags updated



**Example:** ANDS R7, R1, R3

**FlagW<sub>1:0</sub> = 10 AND CondEx = 1 (unconditional) => FlagWrite<sub>1:0</sub> = 10**






# Example: ORR

ALUOp	
RegSrc	
RegW	
ImmSrc	
ALUSrc	
MemW	
MemtoReg	
Branch	
Type	
Funct <sub>0</sub>	
Funct <sub>s</sub>	
Op	




# Example: ORR


Op	Functs	Funct <sub>0</sub>	Type	Branch	MemoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1

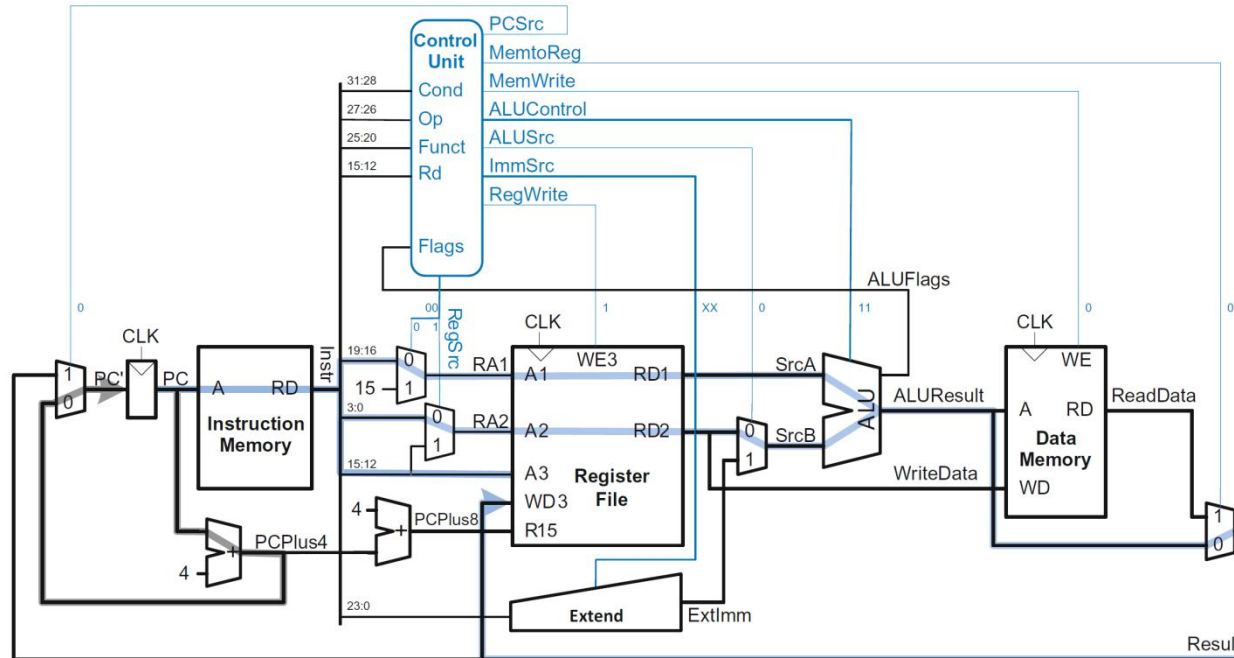


# Example: ORR

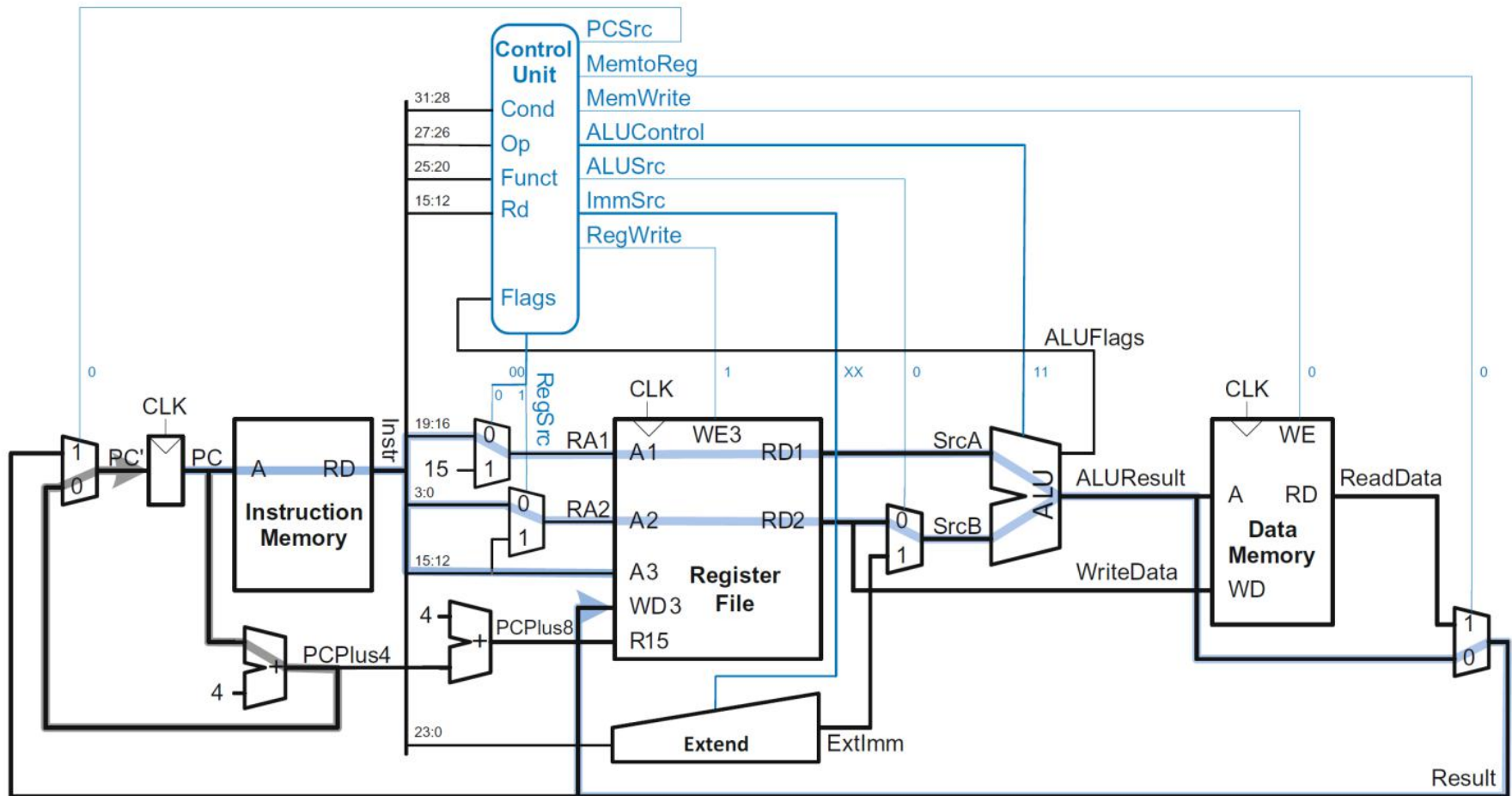


# Extended Functionality: CMP

 

# Extended Functionality: CMP

 


# Extended Functionality: CMP

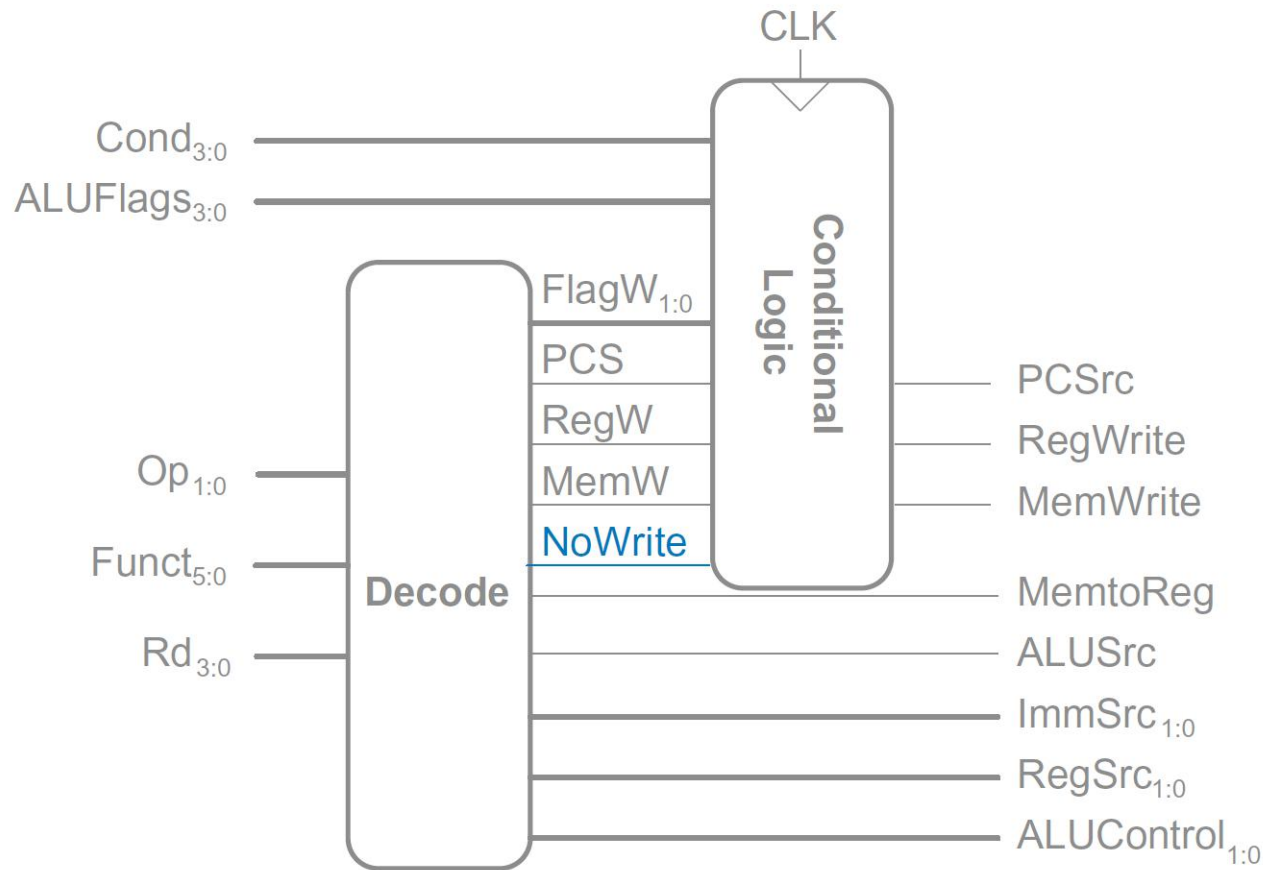

**No change to datapath**



# Extended Functionality: CMP

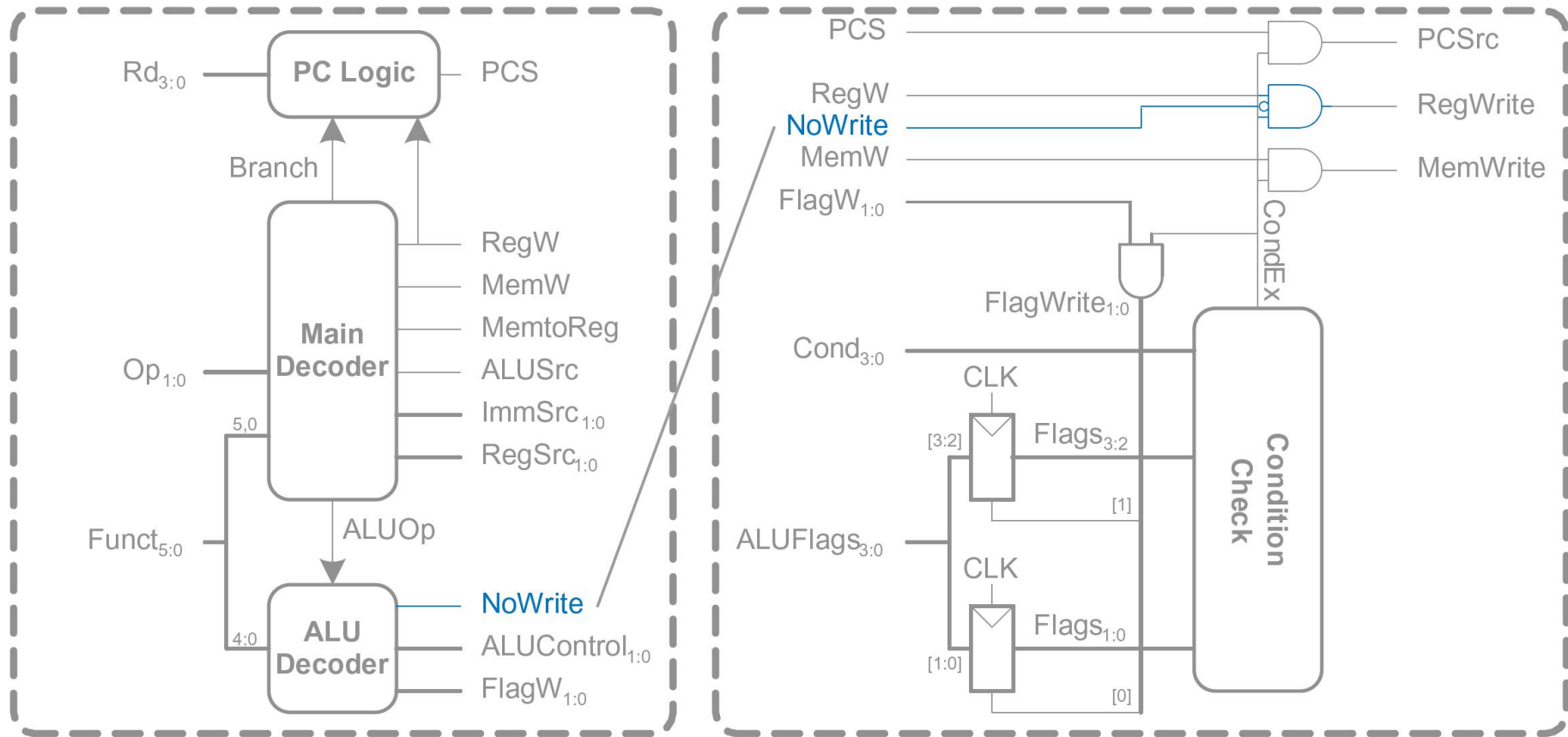


# Extended Functionality: CMP

ALUOp	Func <sub>4:1</sub> (cmd)	Func <sub>0</sub> (S)	Type	ALUControl <sub>1:0</sub>	FlagW <sub>1:0</sub>	NoWrite
0	X	X	Not DP	00	00	0
1	0100	0	ADD	00	00	0
		1			11	0
	0010	0	SUB	01	00	0
		1			11	0
	0000	0	AND	10	00	0
		1			10	0
	1100	0	ORR	11	00	0
		1			10	0
	1010	1	CMP	01	11	1




 
# Extended Functionality: Shifted Register




ADD R7, R2, R12, LSR #5

31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0
14	0	0	4	0	2	7	5	01	2	12
cond	op	I	cmd	S	rn	rd	shamt5	sh		rm


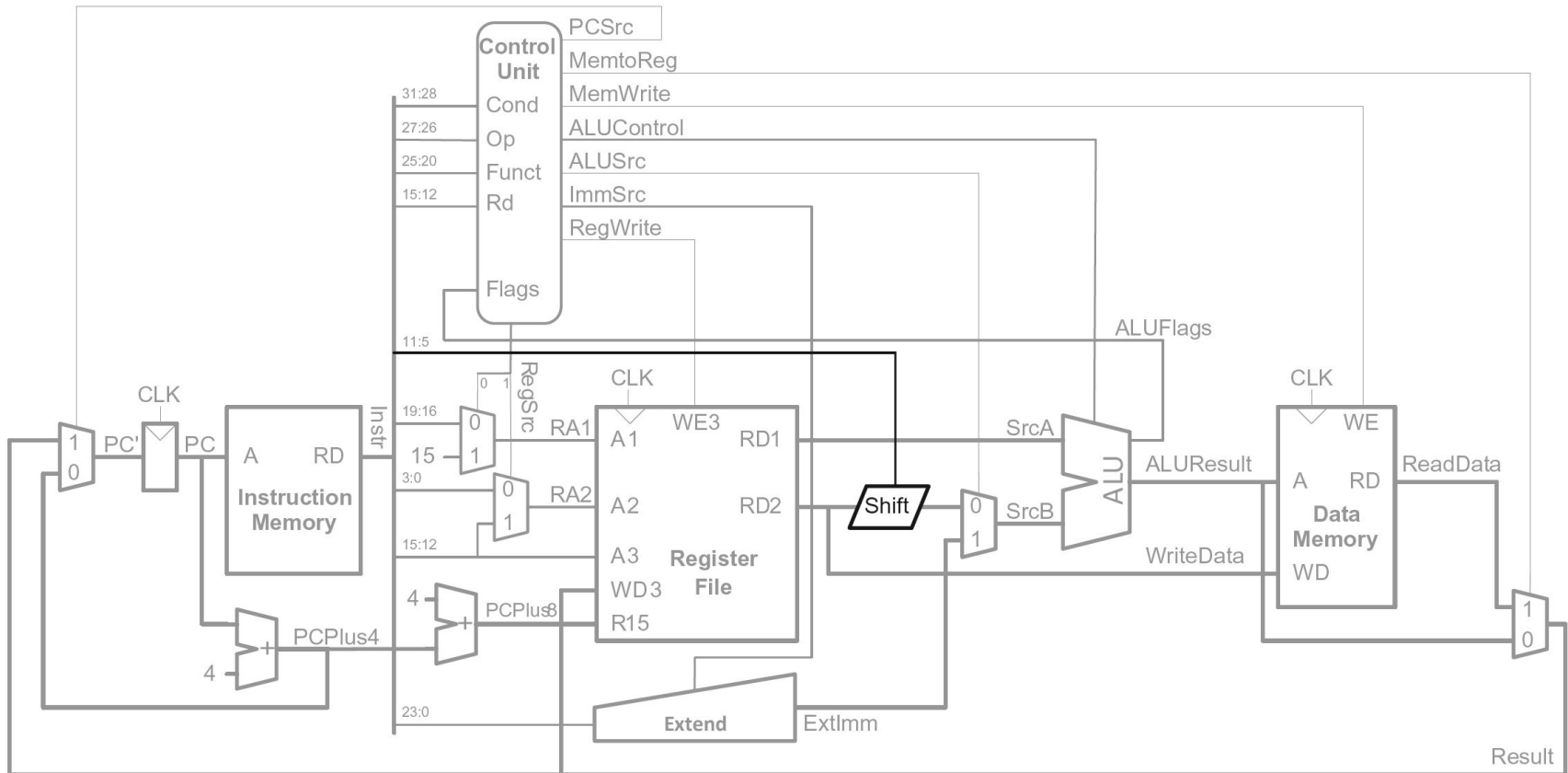
# Extended Functionality: Shifted Register



**No change to controller**



# Review: Processor Performance


## Program Execution Time

$$= (\# \text{instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times T_C$$




# Single-Cycle Performance

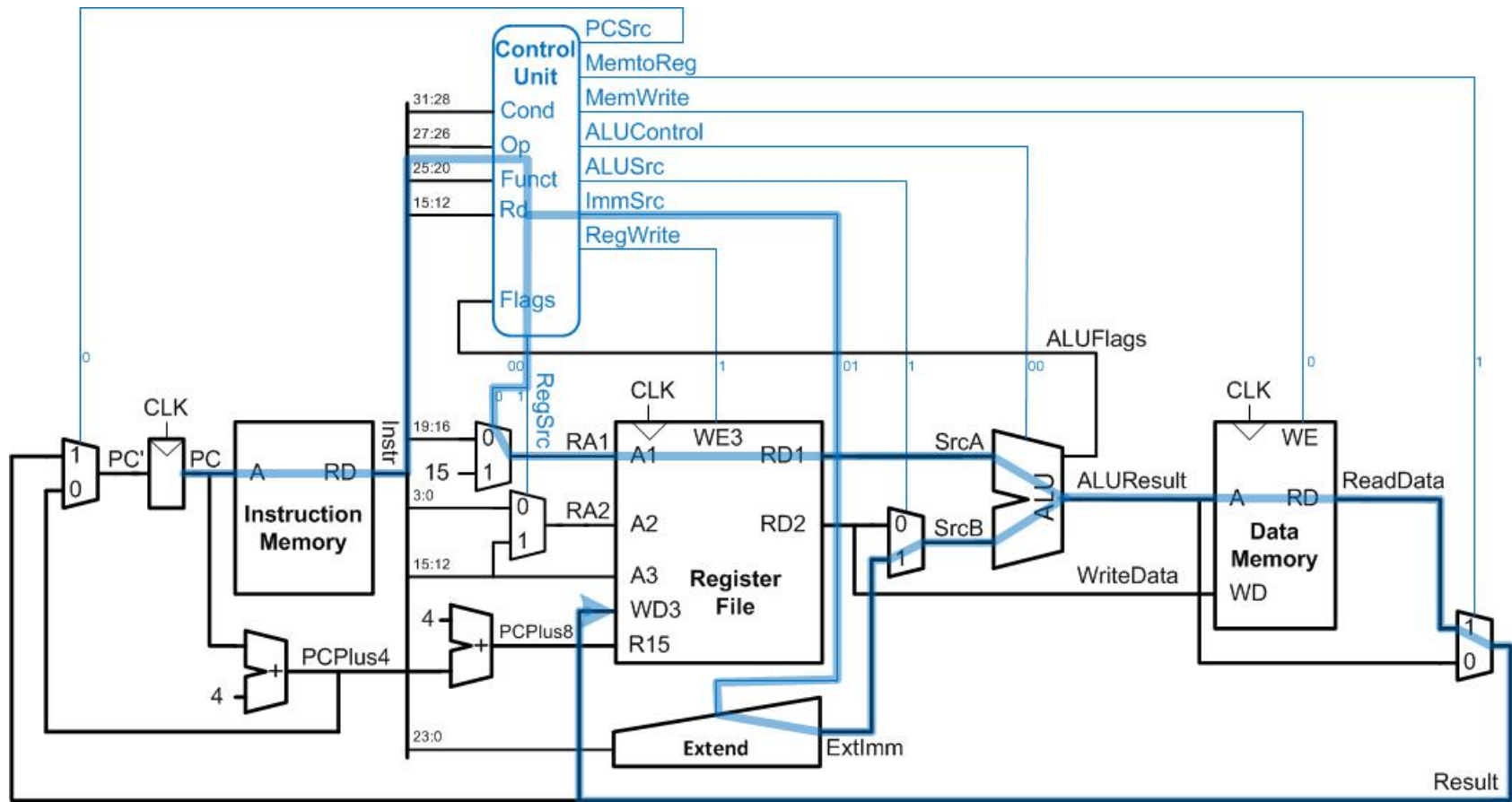

**$T_c$  limited by critical path (?instr?)**



# Single-Cycle Performance

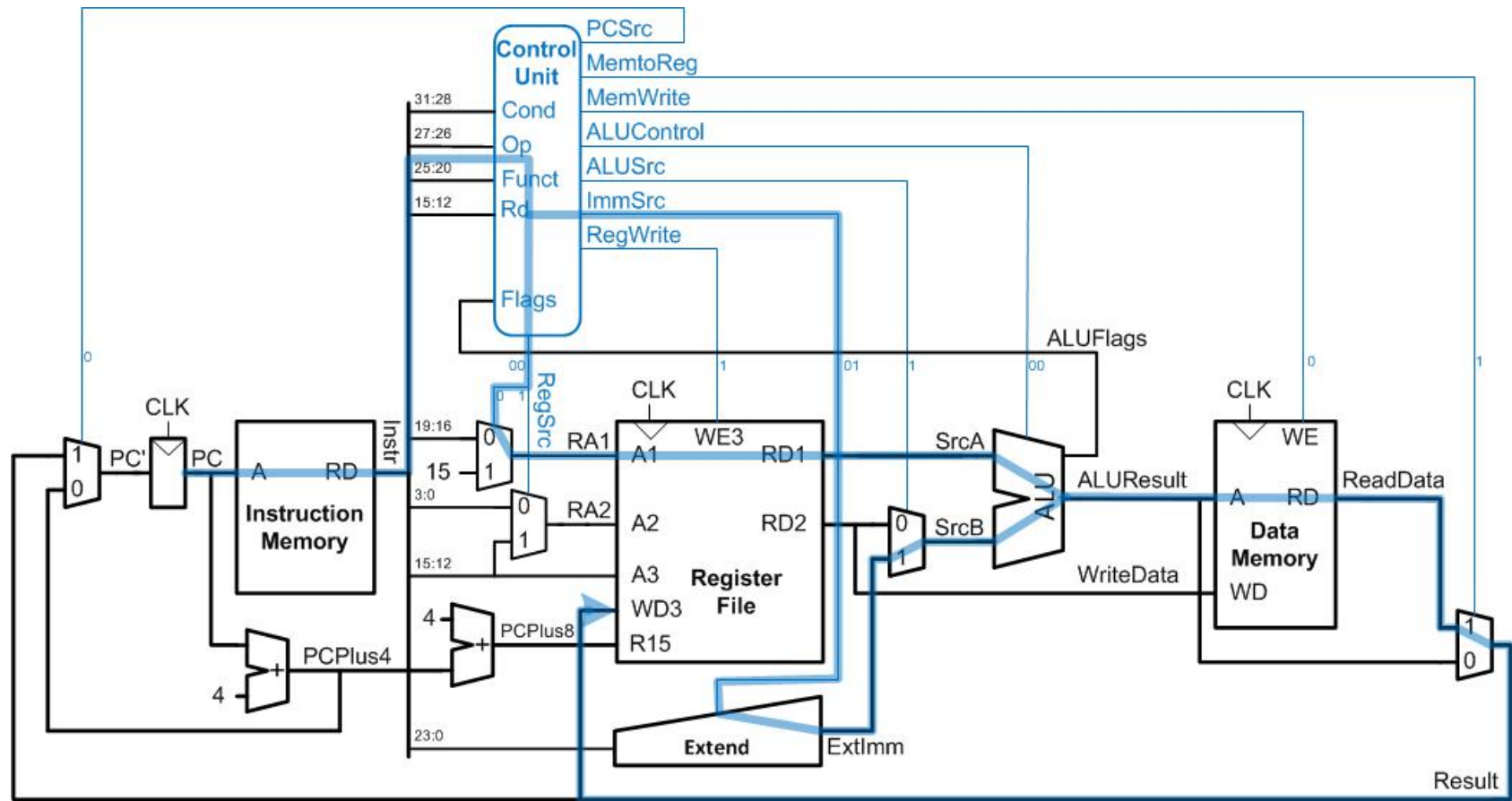

**$T_c$  limited by critical path (LDR)**



# Single-Cycle Performance

- **Single-cycle critical path:**

$$T_{cl} = t_{pcq\_PC} + t_{mem} + t_{dec} + \max[t_{mux} + t_{RFread}, t_{sext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- **Typically, limiting paths are:**

- memory, ALU, register file

- $T_{cl} = t_{pcq\_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$



# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	40
Register setup	$t_{setup}$	50
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	120
Decoder	$t_{dec}$	70
Memory read	$t_{mem}$	200
Register file read	$t_{RFread}$	100
Register file setup	$t_{RFsetup}$	60

$T_{cl} = ?$



# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	40
Register setup	$t_{setup}$	50
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	120
Decoder	$t_{dec}$	70
Memory read	$t_{mem}$	200
Register file read	$t_{RFread}$	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned}
 T_{cl} &= t_{pcq\_PC} + 2t_{mem} + t_{dec} + \\
 &\quad t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\
 &= [50 + 2(200) + 70 + 100 + \\
 &\quad 120 + 2(25) + 60] \text{ ps} \\
 &= \mathbf{840 \text{ ps}}
 \end{aligned}$$





# Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(840 \times 10^{-12} \text{ s}) \\ &= \mathbf{84 \text{ seconds}}\end{aligned}$$



# ARM Single-cycle

